

B. Tech Degree V Semester (Supplementary) Examination July 2009

EC/EI 505 MICRO ELECTRONICS AND INTEGRATED CIRCUITS (2006 Scheme)

Time : 3 Hours

Maximum Marks : 100

PART - A (Answer ALL questions)

(8 x 5 = 40)

- I. (a) List the characteristics of an ideal op-amp.
(b) Explain current to voltage converter using op-amp.
(c) Explain a peak detector using neat sketches.
(d) Draw the transfer characteristics of a Schmitt trigger and explain. What is hysteresis?
(e) Explain the current limiting technique in a 723 voltage regulator.
(f) List the important specifications of ADC/DAC.
(g) Compare monolithic and hybrid IC's and also mention about its application area.
(h) Explain the fabrication of monolithic bipolar npn transistor.

PART - B

(4 x 15 = 60)

- II. Draw the circuit diagram of an instrumentation amplifier. Derive the expression for its output voltage. What are the advantages of instrumentation amplifier. (15)
- OR**
- III. (a) What is meant by input bias current in an op-amp? How it is compensated? (6)
(b) Explain op-amp differentiator and derive the equation for output voltage. (9)
- IV. (a) Explain a log amplifier and show how saturation current and temperature compensation are achieved. (8)
(b) Explain the concept of simulated inductance with neat diagram. (7)
- OR**
- V. (a) With the help of a circuit, explain a 2nd order high pass Butterworth filter and hence derive its transfer function. (8)
(b) Explain the working of a monostable multivibrator using op-amp with diagram. (7)
- VI. Explain a 3 bit flash type analog to digital converter. Discuss its advantages and disadvantages. (15)
- OR**
- VII. (a) What are the features of a 555 timer IC. Draw its functional block diagram and explain. (11)
(b) What o/p voltage would be produced by a 4 bit DAC whose o/p voltage range is 0 to 10V and input binary number is 0111? (4)
- VIII. Discuss thin film and thick film technology. Explain its advantages and applications. (15)
- OR**
- IX. Explain ion implantation in IC fabrication with necessary diagram. (15)

