## SATHYABAMA UNIVERSITY

(Established under section 3 of UGC Act, 1956)

Course & Branch : B.E - ECE Title of the Paper :Network Analysis and Synthesis Max. Marks :80 Sub. Code :6C0053 Time : 3 Hours Date :28/04/2010 Session :FN

> PART - A Answer ALL the Questions

- $(10 \times 2 = 20)$
- 1. Define Driving point impedance.
- Determine the system function if the d.c gain of the system is 10 2. and pole zero plot is as shown in figure.



- 3. State Bartlett bisection theorem.
- 4. Express y parameters in terms of z parameters and h parameters.
- Test whether the polynomial is Hurwitz.  $P(s) = s^3 + 2s^2 + 4s + 2$ . 5.

6. Test whether 
$$F(s) = \frac{3s^2 + 5}{s(s^2 + 1)}$$
 is positive real.

- 7. Compare Butterworth and Chebyshev filters.
- 8. List out Classical Filters.

- 9. List out the Characteristics of Equalizers.
- 10. Compare series and shunt equalizers.

PART – B 
$$(5 \times 12 = 60)$$
  
Answer All the Questions

11. (a) Find the impulse response of the network shown in figure. The excitation is the Voltage v(t) while the response is i(t).



(b) For a given one port network shown in figure, find driving point impedance function Z(s).



12. For the network shown, find z(s) and pole zero diagram.



13. Find the Z Matrix for the two port network shown below.



14. Find y parameters of the two port network shown in figure.



15. Realize the given RC network impedance function using foster form I.  $Z(s) = \frac{(s+1)(s+4)}{S(s+2)}$ .

(or)

- 16. Realize the given RL network impedance function using Cauer Form I.  $Z(s) = \frac{(s+1)(s+3)}{(s+2)(s+4)}$ .
- 17. Design a first order low pass butterworth filter with a cut off frequency of 15.9KHz with a pass band gain of 1.5. Obtain its frequency response,

(or)

- 18. Design a wide band pass filter having fL = 400Hz and fH = 2kHz and pass band gain of 4. Draw the frequency response of the filter and also calculate the Q value of the filter.
- 19. Design a T Pad attenuator to give attenuation of 50Db and to operate into a line of resistance  $600\Omega$ .

(or)

20. Explain in detail about T and Lattice equalizers.