

Code: AE12
Time: 3 Hours

Subject: INSTRUMENTATION AND MEASUREMENT
Max. Marks: 100

DECEMBER 2007

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1. must be written in the space provided for it in the answer book supplied and nowhere else.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or best alternative in the following: (2x10)

- a. The error due to the constant zero offset in a meter can be classified as
- (A) Random error (B) Systematic error
(C) Standard error (D) Uncontrollable error
- b. Kelvin bridge is used mainly for measurement of
- (A) Very small values of resistances
(B) Very high values of resistances that cannot be measured by Wheatstone's bridge
(C) Inductance of transformer windings
(D) Capacitances used in tuning circuits
- c. The value nearest to the resonant frequency of a Wien bridge of an audio frequency generator having its resistors of $10\text{ K}\Omega$ each and capacitors of $0.1\text{ }\mu\text{F}$ each is
- (A) 15.9 Hz (B) 159 Hz
(C) 1.59 kHz (D) 15 kHz
- d. The triggered horizontal sweep in a CRO is generated by
- (A) Pulsing a trigger circuit manually
(B) The signal being measured
(C) A Hall probe
(D) A differentiating circuit at the signal input terminal
- e. The frequency range of a frequency counter can be increased by
- (A) Increasing the clock speed
(B) Increasing the number of digits in the display unit
(C) using a prescaler or divide-by-N counter
(D) An A/D converter of suitable number of output bits
- f. A thermocouple RF ammeter measures a transmitter line current of 1A into a load of $50\text{ }\Omega$. The power delivered to the load is
- (A) 50 W (B) 500 W
(C) 5 W (D) 5 mW
- g. Quieting method is a technique used in
- (A) AM alignment
(B) FM alignment
(C) Transmitter output impedance measurement
(D) Receiver sensitivity measurement
- h. The principle of working of harmonic distortion analyzer is based on
- (A) Heterodyning of two frequencies

- (B) amplification of fundamental frequency
 (C) Suppression of fundamental frequency
 (D) Suppression of harmonics
- i. Which of the following material may be used for obtaining output of electrical potential by applying the mechanical force ?
 (A) Ferrite (B) Alloy of Rhodium and Platinum
 (C) Rochelle Salt (D) Tungsten
- j. A 12-bit successive approximation A/D converter uses a clock of 2 kHz. Its conversion time is
 (A) 3.6 ns (B) 4.8 ms
 (C) 2.4 ms (D) 6ms

**Answer any FIVE Questions out of EIGHT Questions.
 Each question carries 16 marks.**

- Q.2** a. Distinguish between 'passive' and 'active' transducers. Give two examples of each. (6)
- b. Explain the following terms as understood in measurement practice :
 (A) Accuracy (B) Static error
 (C) Repeatability (D) Uncertainty
 (E) Resolution (10)
- Q.3** a. Draw the circuit diagram of amplified current and voltage meter and describe its operation. What are its limitations? (8)
- b. Write the circuit of Maxwell's bridge. Derive the conditions for its balance, and solve the problem given below.
 A Maxwell Bridge is used to measure an inductive impedance Z_x composed of R_x and L_x in series. The bridge shows balance for $R_1 = 450 \text{ k}\Omega$, $C_1 = 0.012 \text{ }\mu\text{F}$, $R_2 = 5 \text{ k}\Omega$ and $R_3 = 100 \text{ k}\Omega$. Find the values of R_x and L_x . (8)
- Q.4** a. Explain 'indirect' method of frequency synthesis' using phase-locked loop. (8)
- b. Write block schematic of digital frequency meter and explain its operation. (8)
- Q.5** a. Show the circuit of a 10-to-1 probe of an oscilloscope and describe its operation. Explain the effects of incorrect setting of the probe taking the example of a fast risetime pulse. (8)
- b. Explain how modulation characteristics of a modulated waveform may be measured using oscilloscope. (8)
- Q.6** a. Delineate, using a circuit schematic, how hysteresis loop of a ring specimen of magnetic material can be traced using a CRO. (8)
- b. How may the RF power be measured by measurement of load voltage? Explain by drawing a circuit scheme. (8)
- Q.7** a. Define 'sensitivity' of a receiver. Explain with diagrams, any one method of measuring receiver sensitivity. (8)
- b. Show a set up of equipments and circuits for FM receiver sweep alignment and describe the procedure for alignment. (8)
- Q.8** a. What is the function performed by a wave analyzer? Draw a block diagram

of heterodyning wave analyzer and explain its working. (8)

- b. Draw a circuit of 4-bit digital-to-analog converter based on R-2R ladder network. Deduce the value of the output voltage as a fraction of the reference voltage for a digital input 0100 (8)

Q.9 a. Define the 'gauge factor' of a resistive strain gauge. Show a Wheatstone bridge circuitry for strain measurement with the facility for 'zero' and 'sensitivity'— adjustment, and describe its operation. (2+6)

- b. Explain the basic principle of working of thermocouples. Give examples of at least two metal pairs useful in constructing thermocouples. (8)