

DiplETE – ET (OLD SCHEME)

Code: DE22
Time: 3 Hours

Subject: INDUSTRIAL ELECTRONICS
Max. Marks: 100

DECEMBER 2010

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after half an hour of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. UJT is generally used for

- (A) Controlling the power (B) Triggering a triac
(C) Triggering an SCR (D) Triggering a Diac.

b. A single-phase full wave half controlled bridge rectifier uses

- (A) 2 SCR's (B) 4 SCR's
(C) 6 SCR's (D) SCR

c. According to their connections, inverters are classified as

- (A) Series inverters. (B) Parallel inverters.
(C) Bridge inverters. (D) All of the above.

d. Thyristors are used to control

- (A) DC separately excited motor (B) DC shunt motor
(C) DC series motor (D) All the above

e. In a single- phase full wave controlled rectifier using centre tap transformer, the voltage across each half secondary is $V_m \sin\omega t$. The peak inverse voltage is

- (A) $2 V_m$ (B) V_m
(C) $0.5 V_m$ (D) $0.25 V_m$

f. When a dc chopper feeds an RL load, the load current, during steady state operation

- (A) Remains constant
(B) Varies between maximum and minimum values
(C) May remain constant or vary
(D) Is constant if R is constant

- g. A cycloconverter can be
- (A) Step down. (B) Step up.
(C) Step down or Step up. (D) Neither of above.
- h. In resistance welding the heat produced is proportional to the
- (A) Current. (B) Square of the current
(C) Voltage (D) Square of the voltage
- i. Induction heating is used for
- (A) Melting (B) Annealing
(C) Forging (D) For all the above.
- j. Inflammable articles like plastic and wooden products etc can be safely heated by using _____ heating.
- (A) Eddy- current (B) Dielectric
(C) Induction. (D) Resistance.

**Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.**

- Q.2** a. Explain series and parallel operation of SCR's with suitable circuit diagrams. (5+5)
- b. Explain, UJT -triggering circuit for an SCR. (6)
- Q.3** a. Draw the waveforms of a single - phase half wave rectifier with R-L load and with freewheeling diode. Explain its operation with a circuit diagram (8)
- b. A single phase rectifier for 10kW rating is required. Thyristors of current rating 50A are to be used. Find the rated voltage of thyristor using a safety factor of 2 if the rectifier is a fullwave using centre tapped transformer, full wave bridge rectifier. Assume R-L load. (8)
- Q.4** a. With the help of a circuit diagram and waveforms, explain the operation of a single- phase half bridge inverter (8)
- b. In a series inverter, $R = 80\Omega$, $L = 8\text{mH}$ and $C = 12\mu\text{F}$. Check whether the circuit will work as a series inverter. Find the maximum output frequency. (8)
- Q.5** a. Explain the different commutation methods for choppers. (10)
- b. Explain the principal of operation of chopper. Give a few applications of choppers. (4+2)
- Q.6** a. What are the losses in dielectric heating? Explain them of them. (8)

- b. With the help of a circuit diagram, explain the principle of induction heating (8)
- Q.7** a. In an induction heating process following parameters were used
 $f = 200 \text{ Hz}$, $B_m = 1 \text{ Wb/m}^2$, $K = 0.83$, $V = 2 \text{ m}^3$.
Calculate the value of heat produced due to eddy current losses in two hours. (8)
- b. Give the applications of resistance welding. Explain the basic circuits of resistance welding. (8)
- Q.8** a. Draw the circuit of Morgan's chopper and describe its operation. (8)
- b. An SCR has a continuous current rating I_{av} of 25A and a dynamic resistance R of 1Ω . If the casing temperature is decreased from 40°C to 30°C by efficient cooling. Calculate the percent increase in the device rating. State the necessary approximation. (8)
- Q.9** Write short notes on:
- (i) Turn off circuits in inverters. (8)
- (ii) Single-phase cycloconverter. (8)