
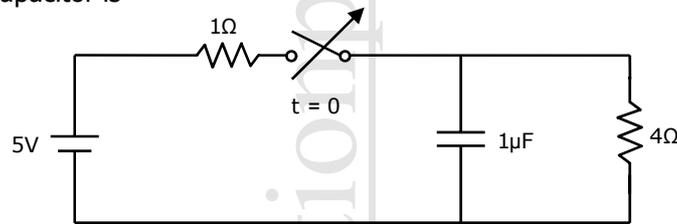


Q. No. 1 – 25 Carry One Mark Each


- The value of the quantity P , where $P = \int_0^1 xe^x dx$, is equal to
(A) 0 (B) 1 (C) e (D) $1/e$
- Divergence of the three-dimensional radial vector field \vec{r} is
(A) 3 (B) $1/r$ (C) $\hat{i} + \hat{j} + \hat{k}$ (D) $3(\hat{i} + \hat{j} + \hat{k})$
- The period of the signal $x(t) = 8\sin\left(0.8\pi t + \frac{\pi}{4}\right)$ is
(A) 0.4π s (B) 0.8π s (C) 1.25s (D) 2.5s
- The system represented by the input-output relationship $y(t) = \int_{-\infty}^{5t} x(\tau) d\tau, t > 0$ is
(A) Linear and causal (B) Linear but not causal
(C) Causal but not linear (D) Neither linear nor causal
- The switch in the circuit has been closed for a long time. It is opened at $t = 0$. At $t = 0^+$, the current through the $1\mu\text{F}$ capacitor is

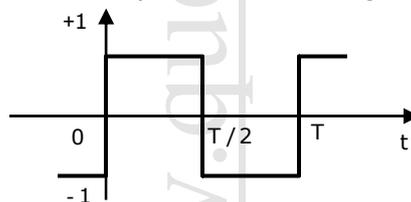


- (A) 0A (B) 1A (C) 1.25A (D) 5A
- The second harmonic component of the periodic waveform given in the figure has an amplitude of



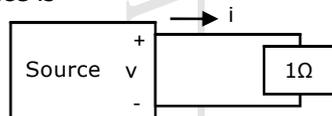- (A) 0 (B) 1 (C) $2/\pi$ (D) $\sqrt{5}$
- As shown in the figure, a 1Ω resistance is connected across a source that has a load line $v + i = 100$. The current through the resistance is



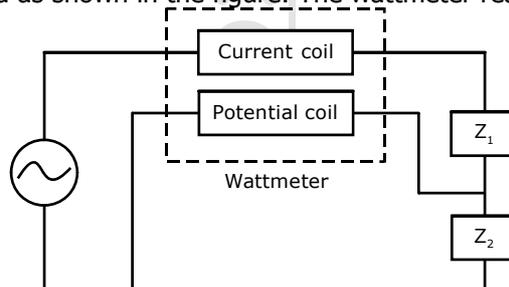
- (A) 25A (B) 50A (C) 100A (D) 200A
- A wattmeter is connected as shown in the figure. The wattmeter reads



- (A) Zero always (B) Total power consumed by Z_1 and Z_2
(C) Power consumed by Z_1 (D) Power consumed by Z_2

9. An ammeter has a current range of 0 - 5 A, and its internal resistance is 0.2Ω . In order to change the range to 0 - 25 A, we need to add a resistance of
 (A) 0.8Ω in series with the meter (B) 1.0Ω in series with the meter
 (C) 0.04Ω in parallel with the meter (D) 0.05Ω in parallel with the meter

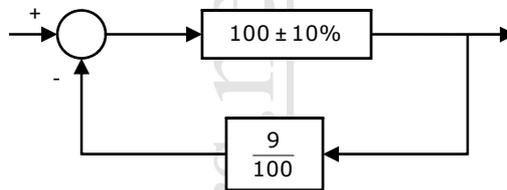
10. As shown in the figure, a negative feedback system has an amplifier of gain 100 with $\pm 10\%$ tolerance in the forward path, and an attenuator of value $9/100$ in the feedback path. The overall system gain is approximately:




- (A) $10 \pm 1\%$ (B) $10 \pm 2\%$ (C) $10 \pm 5\%$ (D) $10 \pm 10\%$

11. For the system $\frac{2}{s+1}$, the approximate time taken for a step response to reach 98% of its final value is
 (A) 1s (B) 2s (C) 4s (D) 8s

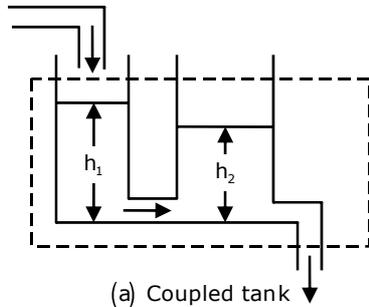12. If the electrical circuit of figure (b) is an equivalent of the coupled tank system of figure (a), then




(a) Coupled tank

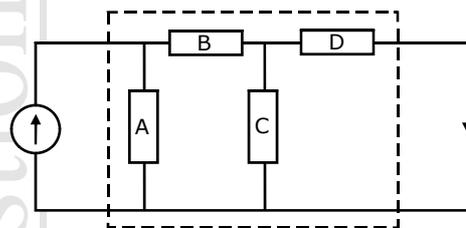

(b) Electrical equivalent


- (A) A, B are resistances and C, D capacitances
 (B) A, C are resistances and B, D capacitances
 (C) A, B are capacitances and C, D resistances
 (D) A, C are capacitances and B, D resistances

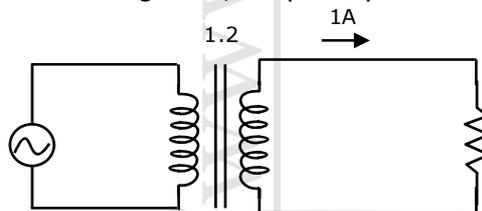13. A single-phase transformer has a turns ratio of 1:2, and is connected to a purely resistive load as shown in the figure. The magnetizing current drawn is 1A, and the secondary current is 1A. If core losses and leakage reactance's are neglected, the primary current is



- (A) 1.41A (B) 2A (C) 2.24 A (D) 3 A

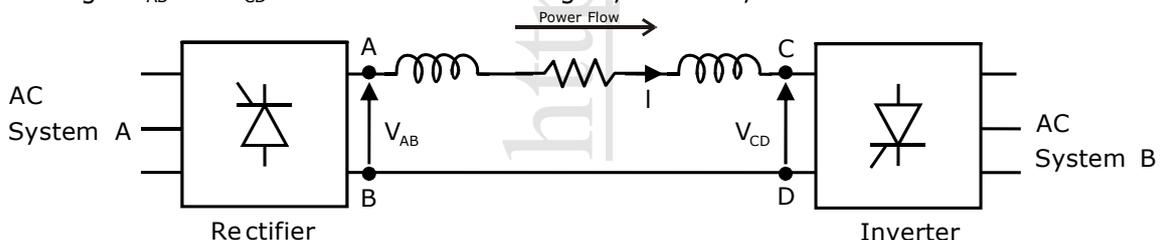14. Power is transferred from system A to system B by an HVDC link as shown in the figure. If the voltages V_{AB} and V_{CD} are as indicated in the figure, and $I > 0$, then




- (A) $V_{AB} < 0, V_{CD} < 0, V_{AB} > V_{CD}$ (B) $V_{AB} > 0, V_{CD} > 0, V_{AB} > V_{CD}$
 (C) $V_{AB} > 0, V_{CD} > 0, V_{AB} < V_{CD}$ (D) $V_{AB} > 0, V_{CD} < 0$

15. A balanced three-phase voltage is applied to a star-connected induction motor, the phase to neutral voltage being V . The stator resistance, rotor resistance referred to the stator, stator leakage reactance, rotor leakage reactance referred to the stator, and the magnetizing reactance are denoted by r_s, r_r, x_s, x_r and X_m , respectively. The magnitude of the starting current of the motor is given by

(A) $\frac{V}{\sqrt{(r_s + r_r)^2 + (x_s + x_r)^2}}$ (B) $\frac{V}{\sqrt{r_s^2 + (x_s + x_m)^2}}$
(D) $\frac{V}{\sqrt{(r_s + r_r)^2 + (x_m + x_r)^2}}$ (C) $\frac{V}{\sqrt{r_s^2 + (x_m + x_r)^2}}$

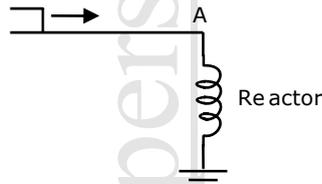
16. Consider a step voltage wave of magnitude 1pu travelling along a lossless transmission line that terminates in a reactor. The voltage magnitude across the reactor at the instant the travelling wave reaches the reactor is



- (A) -1pu (B) 1pu (C) 2pu (D) 3pu
17. Consider two buses connected by an impedance of $(0+j5) \Omega$. The bus 1 voltage is $100 \angle 30^\circ V$, and bus 2 voltage is $100 \angle 0^\circ V$. The real and reactive power supplied by bus 1, respectively, are
(A) 1000W, 268VAr (B) -1000W, -134VAr
(C) 276.9W, -56.7VAr (D) -276.9W, 56.7VAr






18. A three-phase, 33kV oil circuit breaker is rated 1200A, 2000MVA, 3s. The symmetrical breaking current is
(A) 1200 A (B) 3600 A (C) 35 kA (D) 104.8 kA

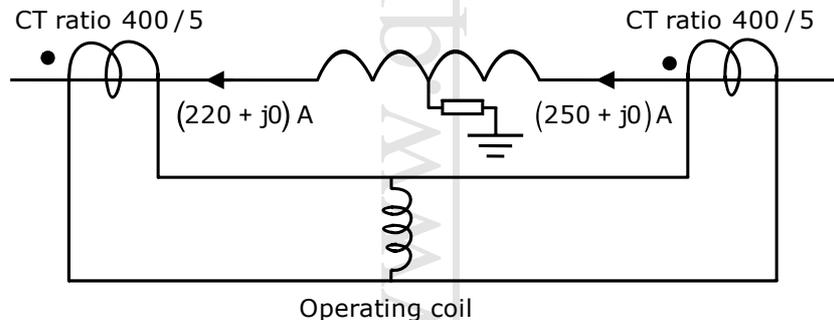19. Consider a stator winding of an alternator with an internal high-resistance ground fault. The currents under the fault condition are as shown in the figure. The winding is protected using a differential current scheme with current transformers of ratio 400/5 A as shown. The current through the operating coil is




- (A) 0.17875 A (B) 0.2 A (C) 0.375A (D) 60 kA

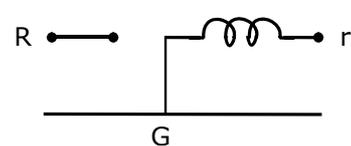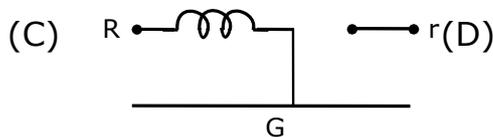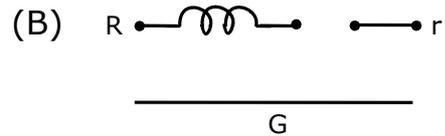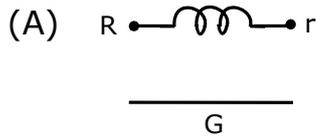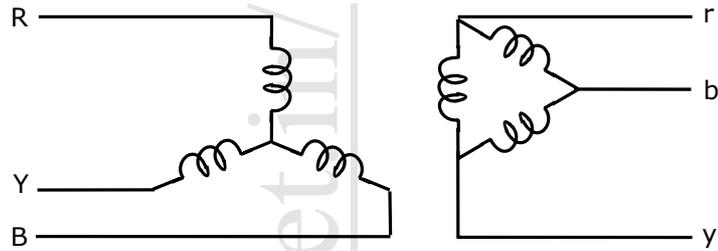20. The zero-sequence circuit of the three phase transformer shown in the figure is




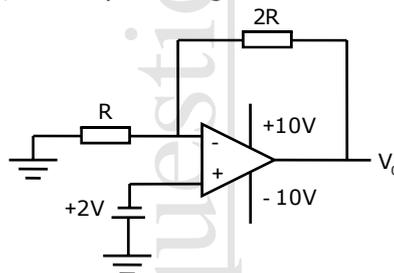21. Given that the op-amp is ideal, the output voltage V_o is




- (A) 4V (B) 6V (C) 7.5V (D) 12.12V

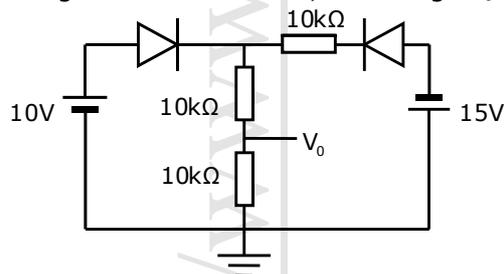22. Assuming that the diodes in the given circuit are ideal, the voltage V_o is





- (A) 4V (B) 5V 10V (C) 7.5V (D) 12.12V

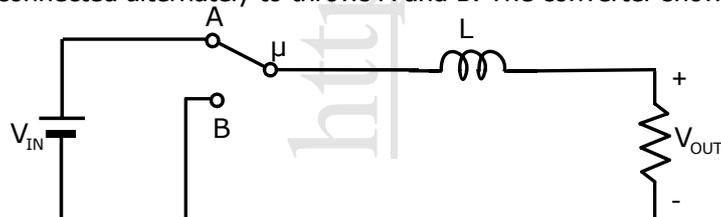23. The power electronic converter shown in the figure has a single-pole double-throw switch. The pole P of the switch is connected alternately to throws A and B. The converter shown is a




- (A) step-down chopper (buck converter)
 (B) half-wave rectifier
 (C) step-up chopper (boost converter)
 (D) full-wave rectifier

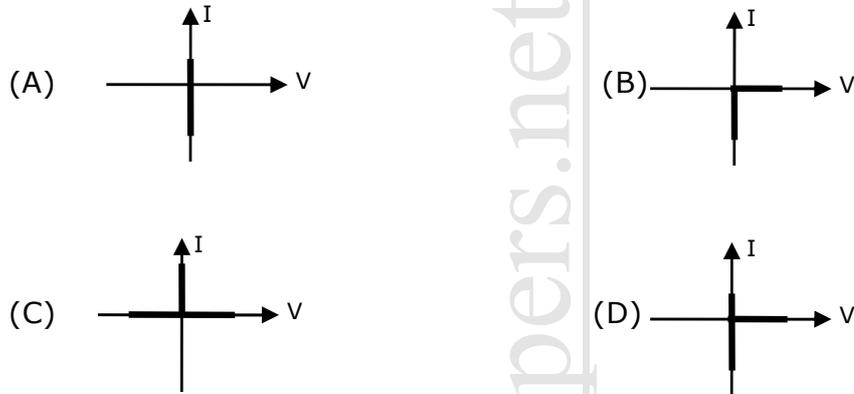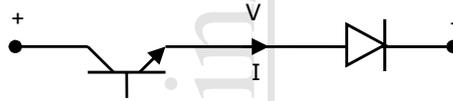24. Figure shows a composite switch consisting of a power transistor (BJT) in series with a diode. Assuming that the transistor switch and the diode are ideal, the I-V characteristic of the composite switch is



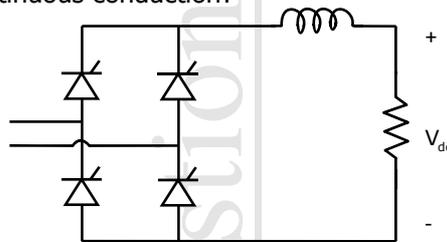25. The fully controlled thyristor converter in the figure is fed from a single-phase source. When the firing angle is 0° , the dc output voltage of the converter is 300V. What will be the output voltage for a firing angle of 60° , assuming continuous conduction?



- (A) 150V (B) 210V (C) 300V (D) $100\pi V$

Q. No. 26 – 51 Carry Two Marks Each


26. At $t = 0$, the function $f(t) = \frac{\sin t}{t}$ has
 (A) a minimum (B) a discontinuity
 (C) a point of inflection (D) a maximum
27. A box contains 4 white balls and 3 red balls. In succession, two balls are randomly selected and removed from the box. Given that the first removed ball is white, the probability that the second removed ball is red is
 (A) $1/3$ (B) $3/7$ (C) $1/2$ (D) $4/7$
28. An eigenvector of $p = \begin{pmatrix} 1 & 1 & 0 \\ 0 & 2 & 2 \\ 0 & 0 & 3 \end{pmatrix}$ is
 (A) $[-1 \ 1 \ 1]^T$ (B) $[1 \ 2 \ 1]^T$ (C) $[1 \ -1 \ 2]^T$ (D) $[2 \ 1 \ -1]^T$
29. For the differential equation $\frac{d^2x}{dt^2} + 6\frac{dx}{dt} + 8x = 0$ with initial conditions $x(0) = 1$ and $\left.\frac{dx}{dt}\right|_{t=0} = 0$, the solution is
 (A) $x(t) = 2e^{-6t} - e^{-2t}$ (B) $x(t) = 2e^{-2t} - e^{-4t}$
 (C) $x(t) = -e^{-6t} + 2e^{-4t}$ (D) $x(t) = e^{-2t} - 2e^{-4t}$

30. For the set of equations, $x_1 + 2x_2 + x_3 + 4x_4 = 2$ and $3x_1 + 6x_2 + 3x_3 + 12x_4 = 6$.

The following statement is true


- (A) Only the trivial solution $x_1 = x_2 = x_3 = x_4 = 0$ exists
 (B) There are no solutions
 (C) A unique non-trivial solution exists
 (D) Multiple non-trivial solutions exist

31. $x(t)$ is a positive rectangular pulse from $t = -1$ to $t = +1$ with unit height as shown in the figure. The value of $\int_{-\infty}^{\infty} |X(\omega)|^2 d\omega$ {where $X(\omega)$ is the Fourier transform of $x(t)$ } is

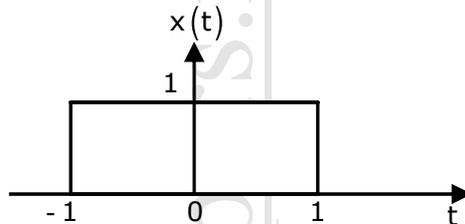


- (A) 2 (B) 2π (C) 4 (D) 4π

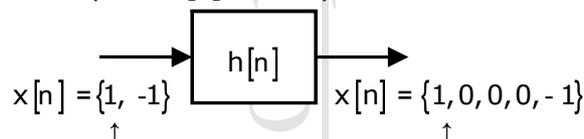32. Given the finite length input $x[n]$ and the corresponding finite length output $y[n]$ of an LTI system as shown below, the impulse response $h[n]$ of the system is




- (A) $h[n] = \{1, 0, 0, 1\}$ (B) $h[n] = \{1, 0, 1\}$
 (C) $h[n] = \{1, 1, 1, 1\}$ (D) $h[n] = \{1, 1, 1\}$

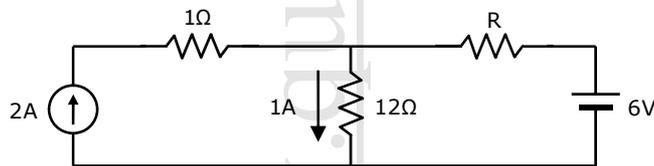33. If the 12Ω resistor draws a current of 1A as shown in the figure, the value of resistance R is




- (A) 4Ω (B) 6Ω (C) 8Ω (D) 18Ω

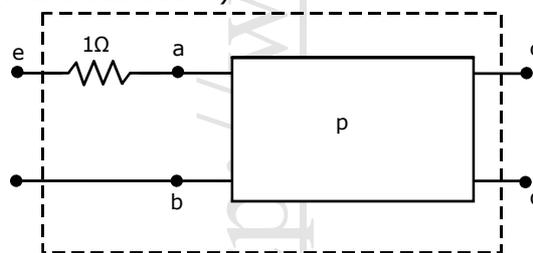34. The two-port network P shown in the figure has ports 1 and 2, denoted by terminals (a, b) and (c, d), respectively. It has an impedance matrix Z with parameters denoted by z_{ij} . A 1Ω resistor is connected in series with the network at port 1 as shown in the figure. The impedance matrix of the modified two-port network (shown as a dashed box) is




- (A) $\begin{pmatrix} z_{11} + 1 & z_{12} + 1 \\ z_{21} & z_{22} + 1 \end{pmatrix}$ (B) $\begin{pmatrix} z_{11} + 1 & z_{12} \\ z_{21} & z_{22} + 1 \end{pmatrix}$
 (C) $\begin{pmatrix} z_{11} + 1 & z_{12} \\ z_{21} & z_{22} \end{pmatrix}$ (D) $\begin{pmatrix} z_{11} + 1 & z_{12} + 1 \\ z_{21} + 1 & z_{22} \end{pmatrix}$

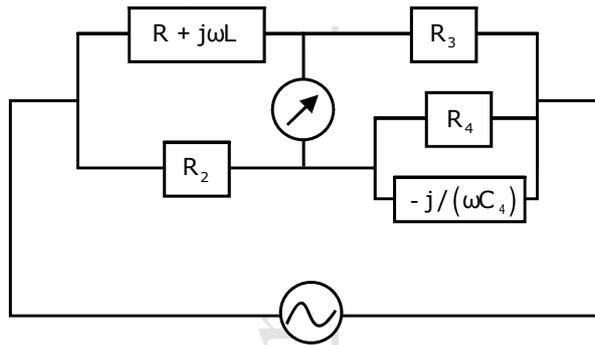35. The Maxwell's bridge shown in the figure is at balance. The parameters of the inductive coil are



- (A) $R = R_2 R_3 / R_4, L = C_4 R_2 R_3$ (B) $L = R_2 R_3 / R_4, R = C_4 R_2 R_3$
(C) $R = R_4 / R_2 R_3, L = 1/(C_4 R_2 R_3)$ (D) $L = R_4 / R_2 R_3, R = 1/(C_4 R_2 R_3)$

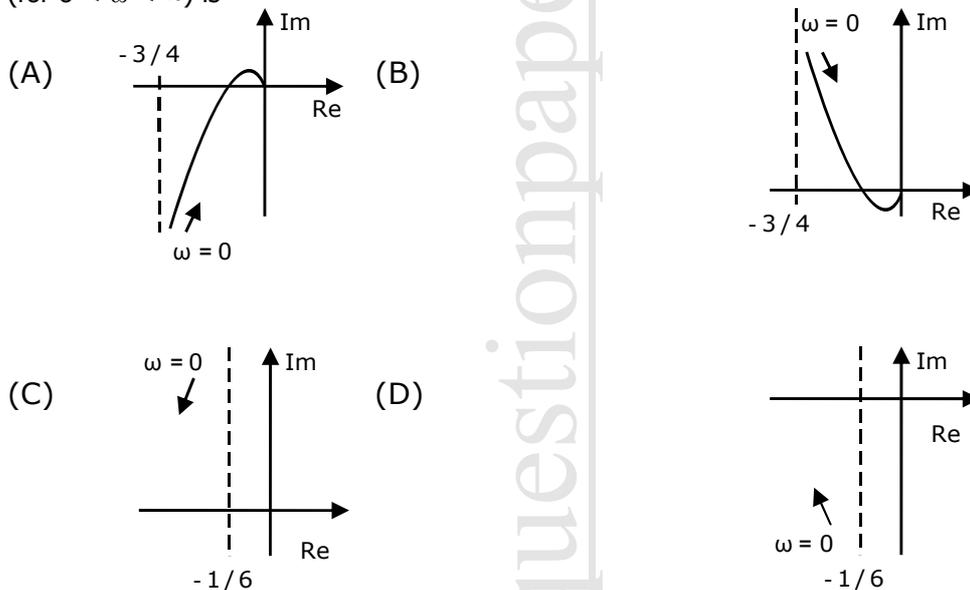36. The frequency response of $G(s) = 1 / [s(s + 1)(s + 2)]$ plotted in the complex $G(j\omega)$ plane (for $0 < \omega < \infty$) is



37. The system $\dot{x} = Ax + Bu$ with $A = \begin{bmatrix} -1 & 2 \\ 0 & 2 \end{bmatrix}, B = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$ is

- (A) stable and controllable (B) stable but uncontrollable
(C) unstable but controllable (D) unstable and uncontrollable

38. The characteristic equation of a closed-loop system is $s(s+1)(s+3)+k(s+2)=0, k>0$. Which of the following statements is true?


- (A) Its roots are always real
(B) It cannot have a breakaway point in the range $-1 < \text{Re}[s] < 0$
(C) Two of its roots tend to infinity along the asymptotes $\text{Re}[s] = -1$
(D) It may have complex roots in the right half plane

39. A 50 Hz synchronous generator is initially connected to a long lossless transmission line which is open circuited at the receiving end. With the field voltage held constant, the generator is disconnected from the transmission line. Which of the following may be said about the steady state terminal voltage and field current of the generator?




- (A) The magnitude of terminal voltage decreases, and the field current does not change
(B) The magnitude of terminal voltage increases, and the field current does not change
(C) The magnitude of terminal voltage increases, and the field current increases
(D) The magnitude of terminal voltage does not change, and the field current decreases

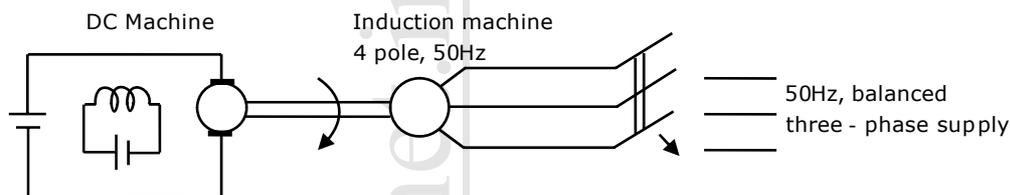
40. A separately excited dc machine is coupled to a 50Hz, three-phase, 4-pole induction machine as shown in the figure. The dc machine is energized first and the machines rotate at 1600 rpm. Subsequently the induction machine is also connected to a 50 Hz, three-phase source, the phase sequence being consistent with the direction of rotation. In steady state,



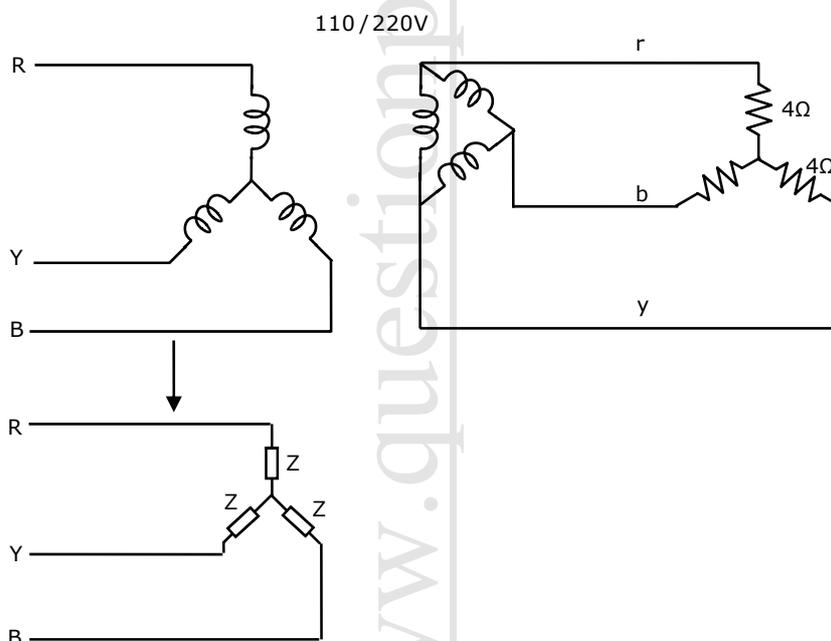- (A) Both machines act as generators
 (B) The dc machine acts as a generator, and the induction machine acts as a motor
 (C) The dc machine acts as a motor, and the induction machine acts as a generator
 (D) Both machines act as motors
41. A balanced star-connected and purely resistive load is connected at the secondary of a star-delta transformer as shown in the figure. The line-to-line voltage rating of the transformer is 110V/220V. Neglecting the non-idealities of the transformer, the impedance 'Z' of the equivalent star-connected load, referred to the primary side of the transformer, is




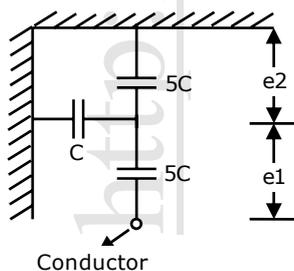- (A) $(3 + j0) \Omega$
 (B) $(0.866 - j0.5) \Omega$
 (C) $(0.866 + j0.5) \Omega$
 (D) $(1 + j0) \Omega$
42. Consider a three-phase, 50Hz, 11kV distribution system. Each of the conductors is suspended by an insulator string having two identical porcelain insulators. The self capacitance of the insulator is 5 times the shunt capacitance between the link and the ground, as shown in the figure. The voltage across the two insulators is




- (A) $e1 = 3.74\text{kV}, e2 = 2.61\text{kV}$
 (B) $e1 = 3.46\text{kV}, e2 = 2.89\text{kV}$
 (C) $e1 = 6.0\text{kV}, e2 = 4.23\text{kV}$
 (D) $e1 = 5.5\text{kV}, e2 = 5.51\text{kV}$

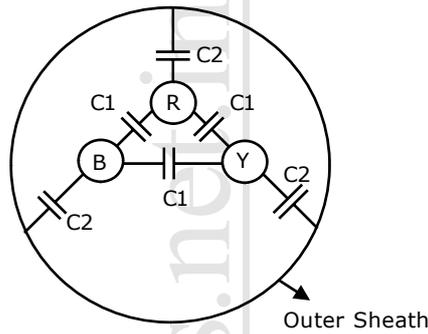43. Consider a three-core, three-phase, 50Hz, 11kV cable whose conductors are denoted as R, Y and B in the figure. The inter-phase capacitance (C_1) between each pair of conductors is $0.2\mu\text{F}$ and the capacitance between each line conductor and the sheath is 0.4 F . The per-phase charging current is



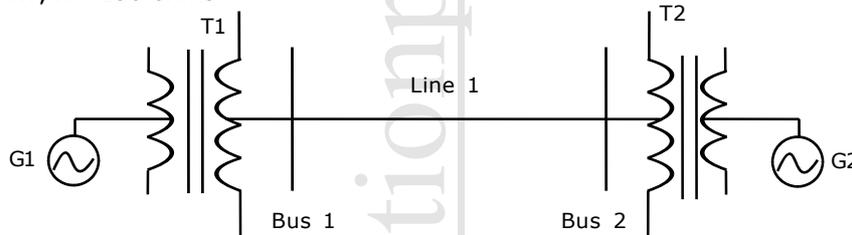
- (A) 2.0A (B) 2.4A (C) 2.7A (D) 3.5A
44. For the power system shown in the figure below, the specifications of the components are the following:
 G1: 25 kV, 100 MVA, $X=9\%$
 G2: 25 kV, 100MVA, $X=9\%$
 T1: 25 kV/220 kV, 90 MVA, $X=12\%$
 T2: 220kV/ 25 kV, 90 MVA, $X=12\%$
 Line1: 220 kV, $X= 150\text{ ohms}$



Choose 25 kV as the base voltage at the generator G1, and 200 MVA as the MVA base. The impedance diagram is



- (A)
 (B)
 (C)
 (D)

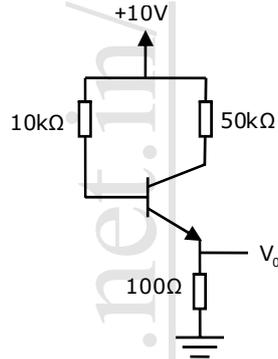45. The transistor circuit shown uses a silicon transistor with $V_{BE} = 0.7V$, $I_C \approx I_E$ and a dc current gain of 100. The value of V_0 is



- (A) 4.65A (B) 5V (C) 6.3V (D) 7.23V

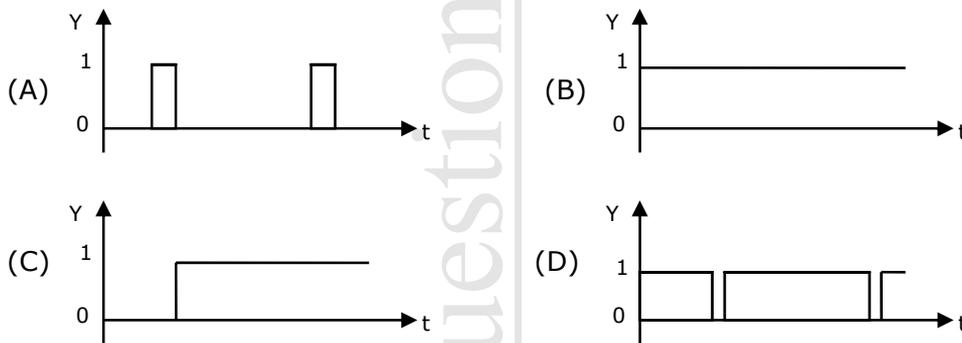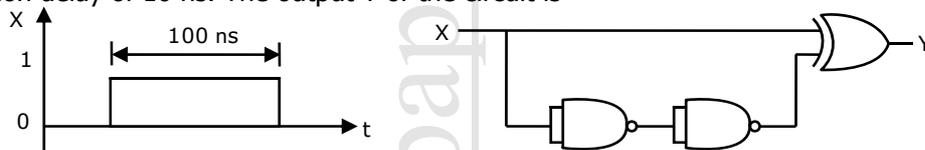46. The TTL circuit shown in the figure is fed with the waveform X (also shown). All gates have equal propagation delay of 10 ns. The output Y of the circuit is



47. When a "CALL Addr" instruction is executed, the CPU carries out the following sequential operations internally:

Note: (R) means content of register R

((R)) means content of memory location pointed to by R


PC means Program Counter

SP means Stack Pointer

- | | | | |
|-----|--|-----|--|
| (A) | (SP) incremented
(PC) ← Addr
((SP)) ← (PC) | (B) | (PC) ← Addr
((SP)) ← (PC)
(SP) incremented |
| (C) | (PC) ← Addr
(SP) incremented
((SP)) ← (PC) | (D) | ((SP)) ← (PC)
(SP) incremented
(PC) ← Addr |

Common Data Questions: 48 & 49

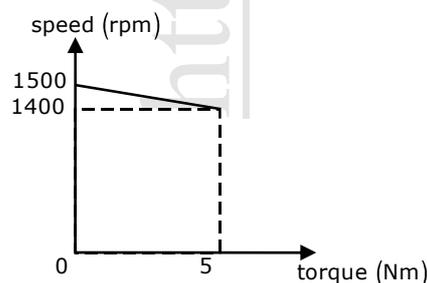
A separately excited DC motor runs at 1500 rpm under no-load with 200 V applied to the armature. The field voltage is maintained at its rated value. The speed of the motor, when it delivers a torque of 5 Nm, is 1400 rpm as shown in the figure. The rotational losses and armature reaction are neglected.



48. The armature resistance of the motor is,
(A) 2Ω (B) 3.4Ω (C) 4.4Ω (D) 7.7Ω
49. For the motor to deliver a torque of 2.5 Nm at 1400 rpm the armature voltage to be applied is
(A) 125.5V (B) 193.3V (C) 200V (D) 241.7V

Common Data Questions: 50 & 51

Given $f(t)$ and $g(t)$ as shown below:

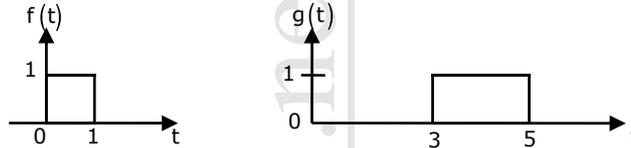

50. $g(t)$ can be expressed as
(A) $g(t) = f(2t - 3)$ (B) $g(t) = f\left(\frac{t}{2} - 3\right)$ (C) $g(t) = f\left(2t - \frac{3}{2}\right)$ (D) $g(t) = f\left(\frac{t}{2} - \frac{3}{2}\right)$
51. The Laplace transform of $g(t)$ is
(A) $\frac{1}{s}(e^{3s} - e^{5s})$ (B) $\frac{1}{s}(e^{-5s} - e^{-3s})$
(C) $\frac{e^{-3s}}{s}(1 - e^{-2s})$ (D) $\frac{1}{s}(e^{5s} - e^{3s})$


Linked Answer Questions: Q.52 to Q.55 Carry Two Marks Each

Statement for Linked Answer Questions: 52 & 53

The following Karnaugh map represents a function F .


F		00	01	11	10
		0	1	1	1
X	0	1	1	1	0
	1	0	0	1	0

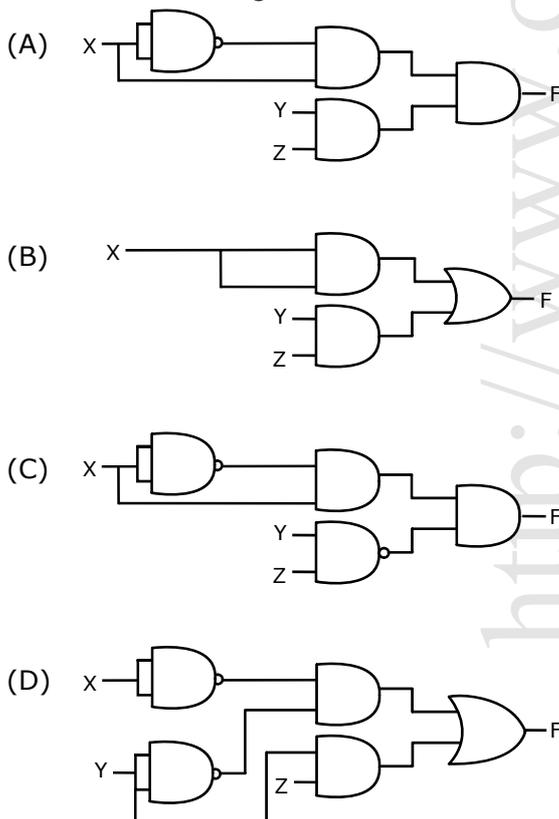52. A minimized form of the function F is
(A) $F = \overline{X}Y + YZ$ (B) $F = \overline{X}\overline{Y} + YZ$ (C) $F = \overline{X}\overline{Y} + Y\overline{Z}$ (D) $F = \overline{X}\overline{Y} + \overline{Y}Z$
53. Which of the following circuits is a realization of the above function F ?



Statement for Linked Answer Questions: 54 & 55

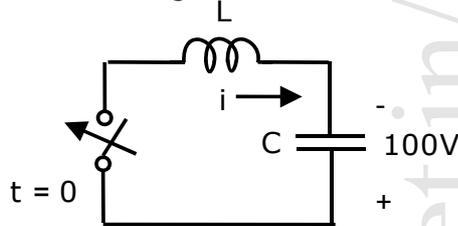
The L-C circuit shown in the figure has an inductance $L = 1\text{mH}$ and a capacitance $C = 10\mu\text{F}$



54. The initial current through the inductor is zero, while the initial capacitor voltage is 100 V. The switch is closed at $t = 0$. The current i through the circuit is:

- (A) $5\cos(5 \times 10^3 t)$ A (B) $5\sin(10^4 t)$ A
(C) $10\cos(5 \times 10^3 t)$ A (D) $10\sin(10^4 t)$ A

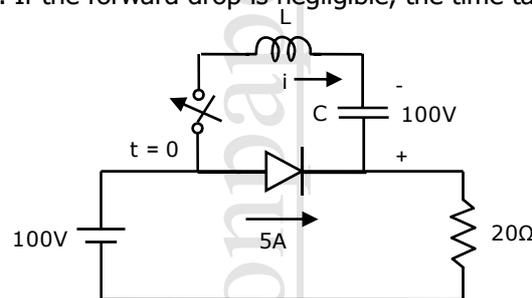55. The L-C circuit of Q54 is used to commutate a thyristor, which is initially carrying a current of 5A as shown in the figure below. The values and initial conditions of L and C are the same as in Q54. The switch is closed at $t = 0$. If the forward drop is negligible, the time taken for the device to turn off is



- (A) $52\mu\text{s}$ (B) $156\mu\text{s}$ (C) $312\mu\text{s}$ (D) $26\mu\text{s}$

Q. No. 56 - 60 Carry one Marks Each

56. 25 persons are in a room. 15 of them play hockey, 17 of them play football and 10 of them play both hockey and football. Then the number of persons playing neither hockey nor football is
(A) 2 (B) 17 (C) 13 (D) 3

57. The question below consists of a pair of related words followed by four pairs of words. Select the pair that best expresses the relation in the original pair.

Unemployed: Worker

- (A) fallow: land (B) unaware: sleeper (C) wit: jester (D) renovated: house

58. Choose the most appropriate word from the options given below to complete the following sentence
If we manage to _____ our natural resources, we would leave a better planet for our children.

- (A) uphold (B) restrain (C) cherish (D) conserve

59. Which of the following options is closest in meaning to the word: Circuitous?

- (A) cyclic (B) indirect (C) confusing (D) crooked

60. Choose the most appropriate word from the options given below to complete the following sentence:

His rather casual remarks on politics _____ his lack of seriousness about the subject.

- (A) masked (B) belied (C) betrayed (D) suppressed

Q. No. 61 - 65 Carry Two Marks Each

61. Hari (H), Gita (G), Irfan (I) and Saira (S) are siblings (i.e. brothers and sisters). All were born on 1st January. The age difference between any two successive siblings (that is born one after another) is less than 3 years. Given the following facts:

- i. Hari's age + Gita's age > Irfan's age + Saira's age
- ii. The age difference between Gita and Saira is 1 year. However Gita is not the oldest and Saira is not the youngest.
- iii. There are no twins. In what order were they born (oldest first)?

- (A) HSI G (B) SGHI (C) IGSH (D) IHSG

62. 5 skilled workers can build a wall in 20days; 8 semi-skilled workers can build a wall in 25 days; 10 unskilled workers can build a wall in 30days. If a team has 2 skilled, 6 semi-skilled and 5 unskilled workers, how long will it take to build the wall?
(A) 20 (B) 18 (C) 16 (D) 15
63. Modern warfare has changed from large scale clashes of armies to suppression of civilian populations. Chemical agents that do their work silently appear to be suited to such warfare; and regretfully, there exist people in military establishments who think that chemical agents are useful tools for their cause. Which of the following statements best sums up the meaning of the above passage:
(A) Modern warfare has resulted in civil strife.
(B) Chemical agents are useful in modern warfare.
(C) Use of chemical agents in warfare would be undesirable
(D) People in military establishments like to use chemical agents in war.
64. Given digits 2,2,3,3,4,4,4,4 how many distinct 4 digit numbers greater than 3000 can be formed?
(A) 50 (B) 51 (C) 52 (D) 54
65. If $137+276=435$ how much is $731+672$?
(A) 534 (B) 1403 (C) 1623 (D) 1513

End of Question Paper