

18/12/09

(Lib)

- Q.B. (1) Question No.1 is **compulsory**.
 (2) Solve any **four** from remaining **six** questions.
 (3) Assume the **suitable** data if **necessary**.

1. (a) Design the W/L ratio of the NMOS transistor used in resistive load inverter with $V_{TO} = 1V$, $V_{DD} = 5V$ and the permissible power dissipation is 0.5 mw , $k'_n = 25 \mu A/V^2$. Assume $V_{OL} = V_{DS} = 0.25V$. 5
 - (b) Arsenic is diffused in silicon with a doping concentration of $5 \times 10^{15} \text{ atoms/cm}^3$. Arsenic doping assumes a Gaussian profile. Arsenic is diffused for 30 minutes and a junction depth of $20 \mu m$ is achieved with a surface concentration of $2 \times 10^{18}/\text{cm}^3$. Find the diffusivity of Arsenic. 5
 - (c) A chip based on CMOS circuit with a supply of $3V$ suppose to work at 10MHz . The chip has 20 devices in it. The total transfer of charge per device is 40nc . Calculate the average power dissipation and also calculate the worst case power dissipation when all the devices switch simultaneously. 5
 - (d) Compare NMOS NAND with NMOS NOR with respect to their (W/L) requirements of driver transistors needed to have symmetric inverter with inverter ratio equal to 1. 5
 2. (a) A device is fabricated with Al gate with work function potential of 0.754 volt . The substrate doping of NMOS is $3 \times 10^{16}/\text{cm}^3$. Determine the thickness of oxide assuming the $Q_{OX} = 1.6 \times 10^{-8} \text{ C/cm}^2$. The inversion occurred at $V_G = 0.65 \text{ V}$. [$n_i = 1.45 \times 10^{10}/\text{cm}^3$, $\epsilon_{OX} = 0.345 \times 10^{-12} \text{ F/cm}^2$, $E_{si} = 1.035 \times 10^{-12} \text{ F/cm}^2$] 10
 - (b) Explain ION implantation and compare it with diffusion clearly stating the advantages and disadvantages. 10
 3. (a) What is band bending? Explain in brief. What is flatband condition and how will you achieve this? 3 + 4 + 3 = 10
 - (b) Design a CMOS NAND gate (two I/p) which is equivalent to the CMOS inverter with $K_R = 2$. 10
 4. (a) Explain the method to design 4:1 MUX using pass transistor logic. Draw the circuit diagram using NMOS pass transistors. Also draw the stick diagram. 10
 - (b) Draw the layout using λ rules for two input NAND gate using NMOS enhancement – depletion technology with $\left(\frac{W}{L}\right)_L = \frac{1}{4}$ and $\left(\frac{W}{L}\right)_D = \frac{1}{2}$. 10
- Take minimum diffusion width = 3λ for any transistor.
5. (a) Compare constant voltage and constant field scaling on the basis of parameters listed :— 10
 - (i) Power density
 - (ii) Driving capacity and
 - (ii) Time delay
 - (iv) Power delay product.
 - (b) State the conditions required for the symmetric CMOS inverter. Prove that $K_R = 1$ with the help of derivation for K_R and conditions for symmetry. 10

6. (a) Explain the concept of pass transistor. What are limitations of PMOS and NMOS pass transistor ? Explain it and also suggest remedy to overcome the limitations.

2 + 6 + 2 = 10

(b) Explain the short channel effects with respect to the following points :—

(i) Subthreshold condition

2

(ii) Channel length modulation effect

3

(iii) Velocity Saturation and Mobility degradation

3

(iv) Drain induced barrier lowering.

2

7. Write short notes on any three of the following :—

20

(a) Butting and Buried Contacts in VLSI

(b) CMOS Latchup and prevention

(c) Custom and semicustom design methods

(d) Photolithography in IC fabrication.