

# GUJARAT TECHNOLOGICAL UNIVERSITY

B.E. Sem-III Remedial Examination March 2010

**Subject code: 130901**

**Date: 10 / 03 / 2010**

**Subject Name: Circuit & Networks**

**Time: 11.00 am – 01.30 pm**

**Total Marks: 70**

**Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Define Charge, Current, Potential difference, Voltage, Node, Loop and Independent source. **07**  
 (b) Using source shifting and source transformation find out the voltage  $V_x$  in the figure. **07**

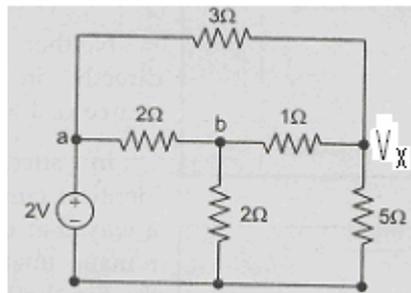


Figure for 1(b)

- Q.2** (a) Explain Substitution theorem. **07**  
 (b) Draw the Thevenin's equivalent of the circuit shown in figure and find current through load resistance (between terminal bb). **07**

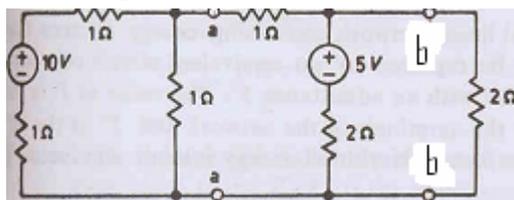


Figure for 2(b)

**OR**

- (b) Find the current in the 5 ohm resistor for the circuit shown in figure using Norton's theorem. **07**

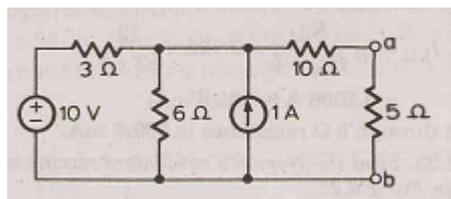


Figure for 2(b)

- Q.3** (a) Explain KCL and KVL using suitable example. **07**  
 (b) Using mesh analysis obtain the current through the 10 V battery for the circuit shown in figure. **07**

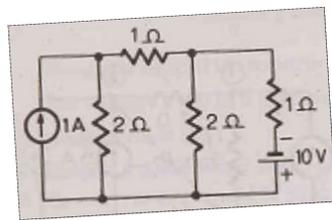


Figure for 3(b)

OR

- Q.3** (a) Explain Millman's theorem. 07  
 (b) Find current and voltage drop through 5 ohm resistor in network shown in figure. 07

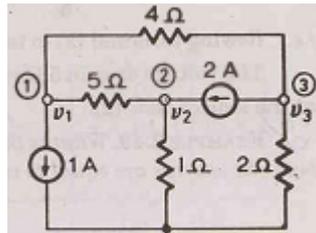


Figure for 3(b)

- Q.4** (a) Derive expression for rise of current and decay of current in RL series circuit excited by DC voltage source. Discuss the role of time constant in each. 07  
 (b) In figure steady state condition is reached with 100 V DC source. At  $t=0$ , switch K is suddenly opened. Find the expression of current through the inductor. Also find current through the inductor at  $t=0.5$  second. 07

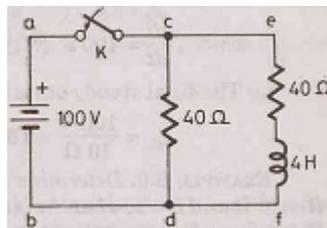


Figure for 4(b)

OR

- Q.4** (a) Draw and explain equivalent circuit of two port network using h-parameters. 07  
 (b) Find the Y-parameter for the circuit shown in figure. 07

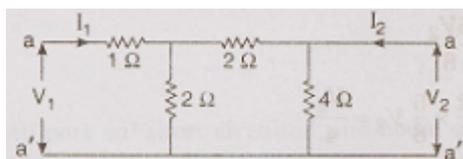


Figure for 4(b)

- Q.5** (a) Derive inter relationship between incidence matrix (A), fundamental tie set matrix ( $B_f$ ) and fundamental cut set matrix ( $Q_f$ ). 07

- (b) For a resistive network shown in figure, draw graph and tree of the network. Also develop the fundamental cut-set matrix. **07**

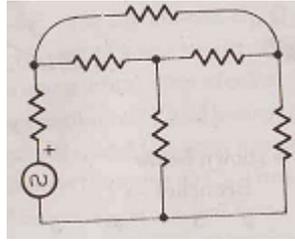


Figure for 5(b)

**OR**

- Q.5** (a) State the procedure to obtain solution of a network using laplace transform method. State advantage of laplace method over classical method. **07**
- (b) What is meant by poles and zeros of a network function? What is the significance of poles and zeros? Discuss the restrictions on locations of poles and zeros of transfer functions. **07**

\*\*\*\*\*