

NPCIL ET Electronics Question Paper 2011 Model Paper with answers

Q. Power diode is generally made from

- a) Silicon
- b) Germanium
- c) Both
- d) None of these

Q. When the both junction of NPN diode is reverse biased, then the diode is in which mode

- a) Active
- b) Cutoff
- c) Saturation
- d) inverted

Q. Which transistor mode gives the inverted output

- a) Common Emitter
- b) Common Base
- c) Common Collector
- d) None of these

Q. Which coupling gives the higher gain in case of amplifier

- a) Capacitor coupling
- b) Impedance coupling
- c) Transformer coupling

Q. Which distortion is least objectionable in audio amplification

- a) Phase
- b) Frequency
- c) Harmonic
- d) Intermediation

Q. A narrow band amplifier has a band pass nearly.....of central frequency

- a) 33.3%
- b) 10%
- c) 50%

Q. Phase shift oscillator consists

- a) RL
- b) RC
- c) RLC

Q. Multivibrator Produces

- a) Sine wave
- b) Square wave
- c) Smooth wave
- d) sawtooth

Q. Convert the 101101 Binary number into octal no

- a) 65

- b) 55
 - c) 51
 - d) 45
- Ans: 55

- Q. 10 in BCD
- a) 10100
 - b) 1100
 - c) 010111
 - d) None of these
- Ans: None of these

- Q. Which PNP device has a terminal for synchronizing purpose
- a) SCS
 - b) Triac
 - c) Diac
 - d) SUS

- Q. Addition of indium in semiconductor crystal makes
- a) PNP
 - b) NPN

- Q. Free electron exists in which band
- a) 1
 - b) 2
 - c) 3
 - d) Conduction band

- Q. Ripple factor of half wave rectifier
- a) 1.21
 - b) 0.48
 - c) 0.5

- Q. Transistor that can be used in enhancement mode
- a) NPN
 - b) UJT
 - c) JFET
 - d) MOSFET

- Q. Following contributes to harmonic distortion in Amplifier
- a) +Ve feedback
 - b) -Ve feedback
 - c) Defective active device

- Q. High cutoff frequency
- a) CB
 - b) CC
 - c) CE

- Q. Which is used as data selector?
- a) Encoder
 - b) Decoder

- c) modulator
- d) Demodulator

Q. Read write capable memory

- a) RAM
- b) ROM
- c) Both
- d) None of these

Q.the radix or base of hexadecimal number system is _____

- a) 8
- b) 16
- c) 5
- d) none of these

Ans: 16

Q.the no of 1's in the binary representation of the expression $162 \cdot 9 + 162 \cdot 7 + 16 \cdot 5 + 3$ are

- a) 10
- b) 23
- c) 6
- d) 4

Q. the no of latches in F/F are _____

- a) 1
- b) 2
- c) 3
- d) 4

Q.how many flip-flops are required to construct Mod -12 counter

- a) 5
- b) 4
- c) 12
- d) none

Ans: 4

Q. which logic gate has the output is compliment of its input _____

- a) OR
- b) AND
- c) NOT
- d) X-OR

Ans: NOT

Q.no.of 2-input multiplexers needed to construct a 210 input multiplexer.....

- a) 12
- b) 31
- c) 20
- d) 16

Q.By adding inverters to the inputs and output of a AND gate we can obtain

- a) OR
- b) AND
- c) NOT
- d) X-OR

Ans: X-OR

Q.how many NAND gates are needed to realize OR gate _____

- a) 1
- b) 2
- c) 3
- d) 4

Ans: 3

Q.which is the first integrated logic family _____

- a) RTL
- b) DTL
- c) TTL
- d) none of these

Q. Which logic gate has output high if and only if all inputs are low _____?

- a) NOR
- b) NAND
- c) X-NOR
- d) AND

Ans: NAND

Q.According to Boolean algebra $1+A+B+C =$

- a) A
- b) A+B+C
- c) 1
- d) none of these

Ans: 1

Q. If $a=0x6db7$ and $b=0x2ae9$ then what is the value of $a \oplus b$ _____

- a) binary number for 1001.1101?
- b) decimal number for 19?
- c) excess-3 code for 29?

Q.what is the value of $A'+1$?

- a) A
- b) A'
- c) 1
- d) none of these

Ans: 1

Q.2 in 4 bit number one bit indicates sign of the number then the locations are from

- a) -8 to 8
- b) -7 to 7
- c) -16 to 16
- d) None

Q.Avalanche photo diode is used when compared to PIN diode bcz

- a)larger band width
- b)high sensitivity
- c)_____
- d)_____

Q. some non zero DC voltage is to RC low pass circuit then the DC voltage in the output contains

- a) Same as in input
- b) Higher than input
- c) Zero
- d) Slightly increases

Q. if the output of the gate is always high then the gates applied to this logic are 0,0

- a) NAND and EX-NOR
- b) NAND and NOR
- c) AND and X-NOR
- d) OR and XOR

Ans: a

Q. Thermal Run away is not possible in FET bcz the flow of

- a) minority carriers
- b) Transconductance
- c) _____
- d) none

Ans : minority carriers

Q. which of the following is/are true about 1's and 2's complements:

- i) In 1's complement form, 0 has two representations
 - ii) in 1's complement, the magnitude of lowest number is equal to the magnitude of highest number
 - iii) In 2's complement, 0 has two representations
- a) i only
 - b) i and ii
 - c) iii only
 - d) all of these

Q. In the hybrid parameter model of a transistor reverse transfer voltage ratio and forward transfer current ratio are respectively given by:

- a) h_{11} and h_{21}
- b) h_{12} and h_{11}
- c) h_{21} and h_{11}
- d) None of these

Q. The largest negative no can be represented with 8 bits in 2's compliment representation?

- a) -256
- b) -255
- c) -127
- d) -128

Ans: -128

Q. How many NAND gates required to implement $AB+CD+EF$

- a) 1
- b) 2
- c) 3
- d) 4

Ans: 4

Q. Transparent latch is seen in which type of flip flop

- a) SR FF
- b) D FF

- c) JK FF
 - d) D FF
- Ans: D FF

Q. Odd parity generator uses which logic?

- a) Digital
- b) Analog
- c) Sequential
- d) none

Q. Which type of ADC is fastest?

- a) SARC
- b) Counter type
- c) Integrated type
- d) Flash

ANS: Flash/Parallel

Q. Which one of the following is fastest read/writable memory?

- a) PROM
- b) EEPROM
- c) Flash
- d) none

Ans: Flash

8. In array programming which one is used

- a) SISD
- b) PISD
- c) MISD
- d) None

Q. Which one of the following has high I/p impedance

- a) CC
- b) CB
- c) CE
- d) None

Q. The maximum time allowed time for each flip flop for a mod 10 synchronous counter if each flip flop delay is 25ns.

- a) 25 ns
- b) 50 ns
- c) 100 ns
- d) none

Q. The resolution for a DAC is given by 0.4% then no. of bits of DAC is

- a) 8- bits
- b) 16- bits
- c) 32- bits
- d) none

Ans: 8- bits

41) The chip capacity is 256 bits, then the no. of chips required to build 1024 B memory is

- a) 32
- b) 16

- c) 15
- d) 4

Q. Which of the following are correct?

- 1) A flip-flop is used to store 1-bit of information
- 2) Race around condition occurs in JK flip flop when both the inputs are 1
- 3) Master slave flip flop is used to store 2 bits of information
- 4) A transparent latch consists of a D- flip flop

- a) 1,2,3
- b) 1,3,4
- c) 1,2,4
- d) 2,3,4

Ans: 1,2,4

Q. output resistance of ideal OP AMP is

- a) 0
- b) 1
- c) infinite
- d) very high

ANS: 0

Q. CMRR of an OP AMP is given as 80db and A_d is 20000. Value of A_{cm} will be

- a) 4
- b) 8
- c) 2
- d) 1

Ans: 2

Q. Si, Ge lie inblock of periodic table

- a) III
- b) V
- c) IV A
- d) IV B

Ans: IV A

Q. to obtain 10 mV resolution on 5 V range how many bit DAC is to be used

- a) 4
- b) 8
- c) 16
- d) 32

Q. % resolution of a 10 bit ADC

- a) 1.588%
- b) 0.392%
- c) 0.0978%
- d) 0.0244%

Ans: 0.0978%

Q. Efficiency of half wave rectifier

- a) 45%
- b) 50%
- c) 86%
- d) 100%