
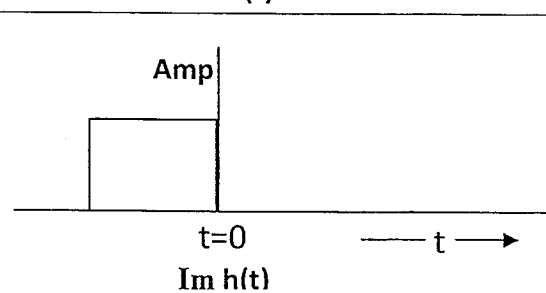
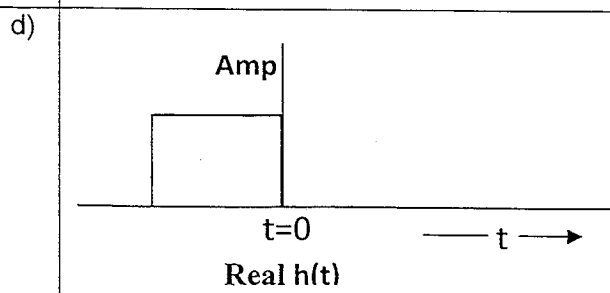
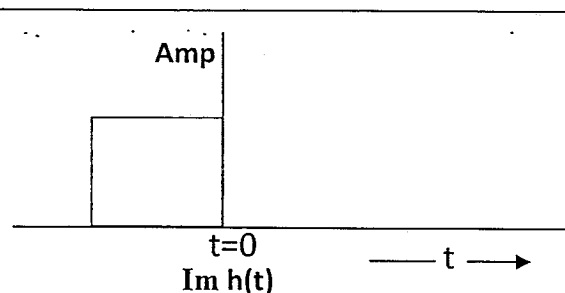
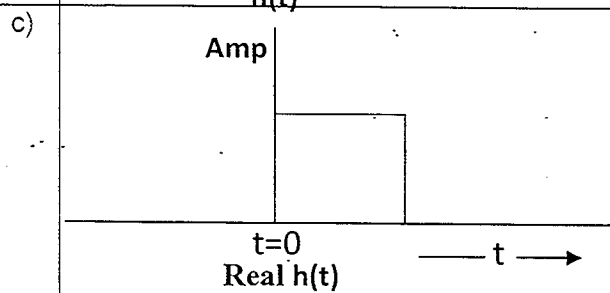
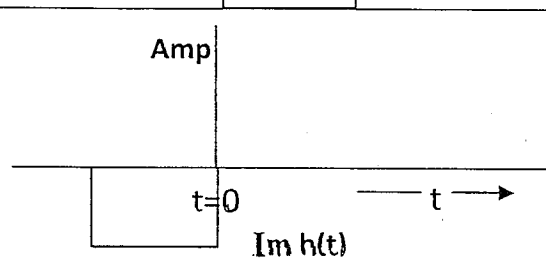
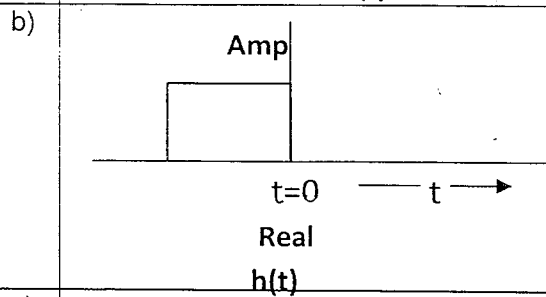
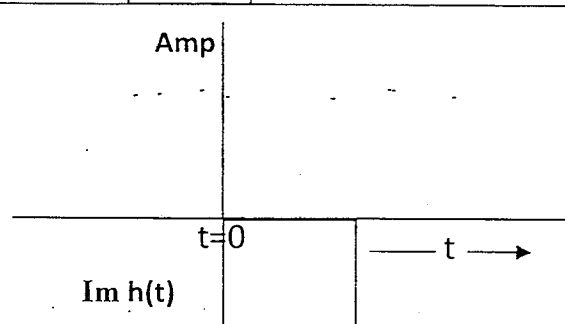
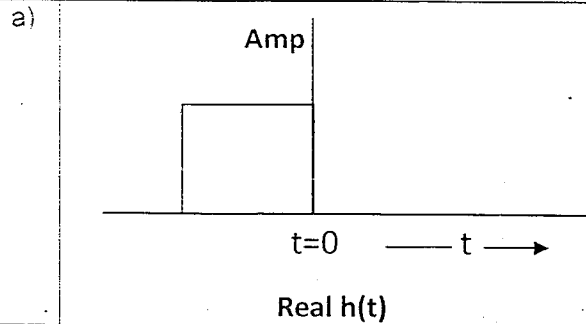
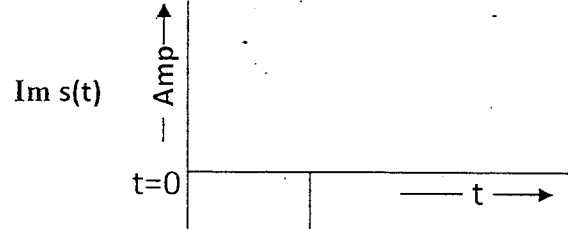


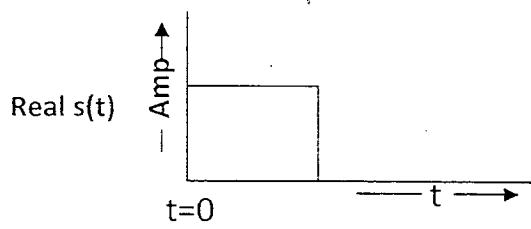1 Determine the matched filter response $h(t)$ for signal $s(t)$ shown below :



ELECTRONICS - 2013 SET -A

6 For an isotropic radiator, electric field intensity at a distance R is measured as 3V/m. What will be the electric field intensity at a distance 3R ?

| | |
|----------------------|----------------------|
| a) 1 V/m | b) $\frac{1}{3}$ V/m |
| c) $\frac{1}{9}$ V/m | d) 3V/m |

7 The logic function implemented by following 4:1 MUX is

| | |
|---------------------------|----------------------------|
| a) $Z = X \text{ and } Y$ | b) $Z = X \text{ or } Y$ |
| c) $Z = X \text{ xor } Y$ | d) $Z = X \text{ xnor } Y$ |

8 Characteristic impedance of a two-wire transmission line at 10KHz is $200-j50$ ohms. Line is terminated in its characteristic impedance, and a 28.28V p-p signal is measured at its input. Determine the real power supplied by the signal source to the line?

| | |
|-----------|-----------|
| a) 0.5 W | b) 0.485W |
| c) 0.47 W | d) 0.25 W |

9 Which is the correct waveform across capacitor in the following circuit?

| | |
|----|----|
| a) | b) |
| c) | d) |

ELECTRONICS – 2013 SET -A

| | | | | |
|----|---|----------------------------------|-----|--|
| 10 | Input voltage applied to a circuit is 1V rms and the output is 1mV rms. Net gain of the circuit is: | | | |
| | a) | + 30dB | b) | - 30dB |
| | c) | - 60dB | d) | + 60dB |
| 11 | Two ideal quantizers A and B have following specifications : A: 5 bit Quantizer with input dynamic range of -1V to +1V with Q1 as quantization noise power B: 8 bit Quantizer with input dynamic range of -0.5V to +0.5V with Q2 as quantization noise power. Then Q1/Q2 will be | | | |
| | a). | 16 | b). | 256 |
| | c) | 64 | d) | 128 |
| 12 | The divergence of magnetic field intensity is | | | |
| | a) | Electric charge density | b) | Electric field intensity |
| | c) | Zero | d) | Conduction current density |
| 13 | A UART is configured to transmit 8 bit data, 1 start bit and 1 stop bit. The serial data output is observed on oscilloscope, which looks like a square wave with frequency of 9600 Hz. What is the baud rate and transmitted data? | | | |
| | a) | Baud rate = 9600, Data = 55h | b) | Baud rate = 19200, Data = 55h |
| | c) | Baud rate = 19200, Data = FFh | d) | Baud rate = 9600, Data = AAh |
| 14 | A transmission line having characteristic impedance of 50ohms has to deliver 10KW power at 100KHz to a load. Maximum permissible value of rms current anywhere along the line is 20A. What is the maximum VSWR that can be tolerated on this line? | | | |
| | a) | 2 | b) | 1 |
| | c) | 3 | d) | 2.5 |
| 15 | Routh Hurwitz criterion is used to determine | | | |
| | a) | Relative stability of the system | b) | Time response of the system |
| | c) | Absolute stability of the system | d) | Roots of the characteristic equation graphically |
| 16 | The decoding circuit shown in the figure is has been used to generate active low chip select signal of memory interfaced to 8 bit microprocessor with 16 bit address bus. What is address range and size of memory? | | | |
| | | | | |
| | a) | D000h to EFFFh , size= 8K Bytes | b) | D000h to DFFFh, size= 4K Bytes |
| | c) | C000h to FFFFh, size= 16K Bytes | d) | E000h to EFFFh, size = 4K Bytes |



| ELECTRONICS - 2013 | | SET -A | |
|--------------------|--|---------------------------------------|--|
| 17 | If the waveguide cross-section of a square waveguide with TE ₁₁ propagation mode is gradually deformed into a circle, then the corresponding circular waveguide mode will be: | | |
| | a) TE ₁₁ | b) TE ₁₀ | |
| | c) TE ₂₁ | d) TE ₁₂ | |
| 18 | What could be the output current rating of following shunt regulator? | | |
| | | | |
| | a) $0 < I_L < 100\text{mA}$ | b) $20\text{mA} < I_L < 100\text{mA}$ | |
| | c) $0 < I_L < 50\text{mA}$ | d) $10\text{mA} < I_L < 100\text{mA}$ | |
| 19 | An FM-CW (Frequency Modulated – Continuous Wave) Radar is essentially | | |
| | a) Bistatic | b) Monostatic | |
| | c) Can operate either as monostatic or as bistatic | d) None of the above | |
| 20 | The flux in a magnetic core is sinusoidally varying at 200 Hz. The maximum flux density is 2 Tesla and eddy current loss is 15 W. If the frequency is raised to 400 Hz and maximum flux density reduced to 1 Tesla, the eddy current loss will | | |
| | a) Reduce to half | b) Get doubled | |
| | c) Reduce to one-fourth | d) Remain same | |
| 21 | The electric field intensity E and magnetic field intensity H are coupled and propagating in free space in x and y direction respectively, the Poynting vector is given by | | |
| | a) $EH\hat{x}$ | b) $EH\hat{y}$ | |
| | c) $EH\hat{xy}$ | d) None of the above | |
| 22 | If x and y are two random signals with zero mean Gaussian distribution having identical standard deviation, the phase angle between them is | | |
| | a) Zero mean Gaussian distributed | b) Uniform between $-\pi$ and π | |
| | c) Uniform between $-\pi/2$ and $\pi/2$ | d) Non-zero mean Gaussian distributed | |
| 23 | The current flowing through a capacitor in an AC circuit is : | | |
| | a) Non-existent | b) Conduction current | |
| | c) Displacement current | d) None of the above | |



ELECTRONICS – 2013

SET -A


| | | | | |
|----|--|---|----|-------------------------------------|
| 24 | Which of the following is the Boolean function for Majority Voting, assuming A,B,C are inputs and Y is output? | | | |
| | a) | $Y = AB + AC + CB$ | b) | $Y = A+B+C$ |
| | c) | $Y = ABC$ | d) | $Y = AB + BC$ |
| 25 | For broadside antenna array, the largest possible spacing between the antenna elements without any grating lobes is | | | |
| | a) | $\lambda/2$ | b) | λ |
| | c) | 2λ | d) | None of the above |
| 26 | For the 8085 assembly language program given below, the content of the accumulator after the execution of the program is 3000 MVI A, 45H 3002 MOV B, A 3003 STC 3004 CMC 3005 RAR 3006 XRA B | | | |
| | a) | 00H | b) | 45H |
| | c) | 67H | d) | E7H |
| 27 | Conduction angle of a Class AB amplifier is: | | | |
| | a) | $<180^\circ$ | b) | Between 180° and 360° |
| | c) | 360° | d) | 90° |
| 28 | For non dispersive medium | | | |
| | a) | Phase velocity $>$ Group velocity | b) | Phase velocity $<$ Group velocity |
| | c) | Phase velocity = Group velocity | d) | None of the above |
| 29 | Schottky clamping is resorted in TTL gates | | | |
| | a) | to reduce propagation delay | b) | to increase noise margins |
| | c) | to increase packing density | d) | to increase fan-out |
| 30 | At cut-off frequency, the phase velocity of a waveguide is | | | |
| | a) | Zero | b) | Infinite |
| | c) | Finite | d) | None of the above |
| 31 | A Zener diode, when used in voltage stabilization circuits, is biased in | | | |
| | a) | reverse bias region below the breakdown voltage | b) | reverse breakdown region |
| | c) | forward bias region | d) | forward bias constant current mode |



INDIAN SPACE RESEARCH ORGANISATION

Page 6 of 18

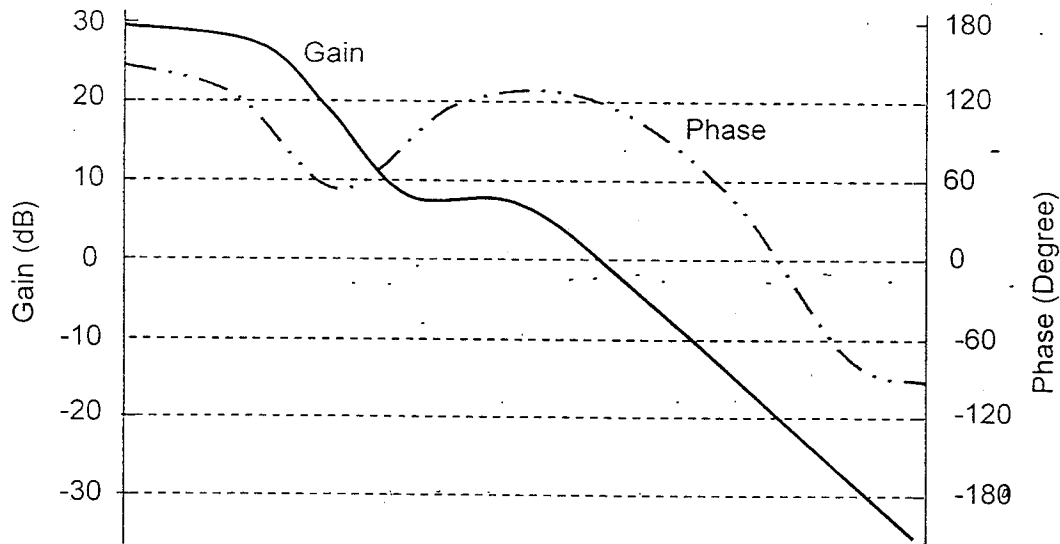32 The closed loop frequency response of a dc-dc converter is shown in following figure. What are the gain and phase margins?



- | | | | |
|----|------------|----|------------|
| a) | 20dB, 80° | b) | 26dB, 80° |
| c) | 20dB, 120° | d) | 26dB, 120° |

33 If for a silicon npn transistor, the base-to-emitter voltage (V_{BE}) is 0.7V and the collector-to-base voltage (V_{CB}) is 0.2 V, then the transistor is operating in the

- | | | | |
|----|---------------------|----|-----------------|
| a) | normal active mode | b) | saturation mode |
| c) | inverse active mode | d) | cutoff mode |

34 3 port Circulator is

- | | | | |
|----|-------------------------|----|---------------------------|
| a) | Reciprocal, matched | b) | Non reciprocal, unmatched |
| c) | Non reciprocal, matched | d) | Reciprocal, unmatched |

35 An 8 bit ripple counter and an 8 bit synchronous counter are made using flip flops having a propagation delay of 10 ns each. If the worst case delay in the ripple counter and the synchronous counter be R and S respectively, then

- | | | | |
|----|--|----|--|
| a) | $R = 10 \text{ ns}, S = 80 \text{ ns}$ | b) | $R = 40 \text{ ns}, S = 10 \text{ ns}$ |
| c) | $R = 10 \text{ ns}, S = 10 \text{ ns}$ | d) | $R = 80 \text{ ns}, S = 10 \text{ ns}$ |

36 Gain of an RC low pass filter having a time constant ' τ ' and frequency ' ω ' is:

- | | | | |
|----|--|----|--|
| a) | $\sqrt{1 + (\omega\tau)^2}$ | b) | $1/\sqrt{1 + (\omega\tau)^2}$ |
| c) | $\omega\tau/\sqrt{1 + (\omega\tau)^2}$ | d) | $\omega\tau/\sqrt{1 - (\omega\tau)^2}$ |



| | | | | |
|----|--|--------------------------------|--|--|
| 37 | For a directional coupler, the quantities I (isolation in dB), D (directivity in dB), C (coupling in dB) are related by | | | |
| | a) $I=C/D$ | b) $I = D - C$ | | |
| | c) $I = D + C$ | d) $I= D/C$ | | |
| 38 | The two numbers represented in signed 2's complement form are $P = 11101101$ and $Q = 11100110$. If Q is subtracted from P , the value obtained in signed 2's complement is | | | |
| | a) 1000001111 | b) 00000111 | | |
| | c) 11111001 | d) 111111001 | | |
| 39 | Depletion type MOSFET operates in : | | | |
| | a) Depletion Model only | b) Enhancement Mode only | | |
| | c) Both depletion and enhancement mode | d) None of the above | | |
| 40 | Electric Field and Magnetic Field are perpendicular to each other in : | | | |
| | a) Klystron | b) Magnetron | | |
| | c) TWTA | d) All of the above | | |
| 41 | A linear regulator is attempted using discrete components as shown below. What is the output voltage? | | | |
| | | | | |
| | a) 9.3 V | b) 7.5 V | | |
| | c) 0 V | d) 2.5 V | | |
| 42 | If range of a radar is to be doubled, the peak transmit power of the radar has to be : | | | |
| | a) Increased by a factor of 2 | b) Increased by a factor of 4 | | |
| | c) Decreased by a factor of 4 | d) Increased by a factor of 16 | | |
| 43 | The electric field measured in the far field of an antenna at a distance of 50m is 1V/m. The average power densities at a distance of 500m from the antenna is | | | |
| | a) $26.6\mu W/m^2$ | b) $0.1\mu W/m^2$ | | |
| | c) $10\mu W/m^2$ | d) $13.3\mu W/m^2$ | | |

ELECTRONICS – 2013

SET -A


| | | |
|----|---|--|
| 44 | If a counter having 10 Flip Flops is initially at 0, what count will it hold after 2060 pulses ? | |
| | a) 000 000 1100 | b) 000 001 1100 |
| | c) 000 001 1000 | d) 000 000 1110 |
| 45 | For a frequency modulated signal represented by $s(t)=10\sin(6 \times 10^8 t + 2\sin 100\pi t)$. The maximum frequency deviation in the carrier from its unmodulated frequency is: | |
| | a) 990Hz | b) 100Hz |
| | c) 50Hz | d) 200Hz |
| 46 | For which of the following conditions, the circuit shown below will function as precision full wave rectifier? | |
| | | |
| | a) $R_1 = R_2 = R$ | b) $R_1 = R_3 = R$ |
| | c) $R_2 = 2R_1$ | d) $R_1 = R_2 = R_3$ |
| 47 | In a monostatic radar, if the antenna aperture is doubled, then the radar range will | |
| | a) Reduce by a factor of 2 | b) Increase by a factor of 2 |
| | c) Reduce by a factor of $\sqrt{2}$ | d) Increase by a factor of $\sqrt{2}$ |
| 48 | The disadvantage of single stub matching is that | |
| | a) Every load needs a new stub position | b) Only shunt stub should be used |
| | c) Only resistive load can be matched | d) Useful only in two wire transmission line |
| 49 | A certain antenna with an efficiency of 95% has maximum radiation intensity of 0.5 W/sr. The directivity of the antenna fed by input power of 0.4 W | |
| | a) 16.53 | b) 12.2 |
| | c) 10.36 | d) 11.31 |
| 50 | A memory system of size 16 K bytes is required to be designed using memory chips which have 12 address lines and 4 data lines each. Then number of such chips required to design the memory system is | |
| | a) 2 | b) 4 |
| | c) 8 | d) 16 |



INDIAN SPACE RESEARCH ORGANISATION

Page 9 of 18

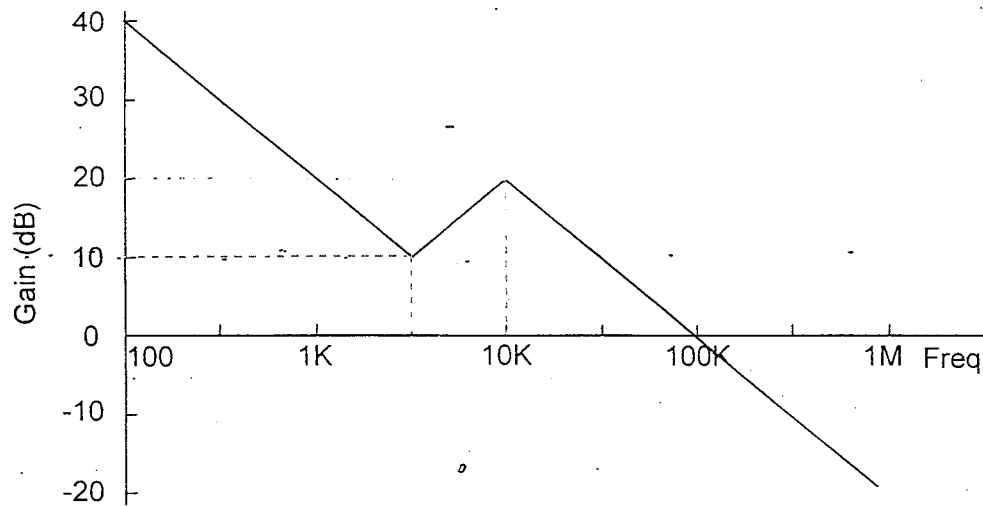51 In the asymptotic bode plot of a transfer function of a closed loop system shown below, the number of poles and zeros are,




- | | | | |
|----|----------------|----|----------------|
| a) | 3 pole, 2 zero | b) | 2 pole, 2 zero |
| c) | 2 pole, 1 zero | d) | 3 pole, 1 zero |

52 Plane Wave travelling in free space has an average Poynting vector of $3W/m^2$. Average energy density (nJ/m^3) of the wave is:

- | | | | |
|----|----|----|---|
| a) | 10 | b) | 5 |
| c) | 1 | d) | 3 |

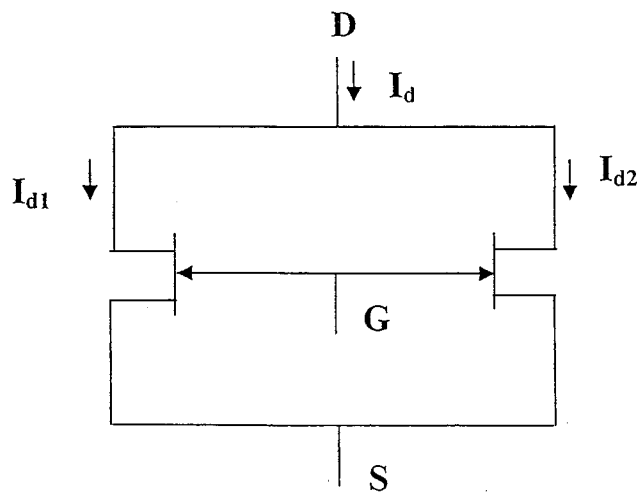53 For two identical n-channel JFET's connected in parallel as shown in fig. below, the pinch-off voltage of equivalent JFET is :



ELECTRONICS – 2013

SET -A

| | | | | |
|----|--|------------------------------|----|------------------------------|
| | a) | Doubled | b) | Becomes half |
| | c) | Remains same | d) | None of the above |
| 54 | The velocity at which a sinusoidal signal of 10^9 rad/s travels down a loss-less transmission line for which $L=0.4 \mu\text{H/m}$ and $C=40 \text{ pF/m}$ is | | | |
| | a) | 2.36×10^8 m/s | b) | 2.5×10^8 m/s |
| | c) | 5×10^9 m/s | d) | 4.5×10^9 m/s |
| 55 | The Maxwell's equation $\nabla \times \vec{E} = -\frac{\partial \vec{B}}{\partial t}$ is obtained from : | | | |
| | a) | Ampere's Law | b) | Faraday's Law |
| | c) | Lenz's Law | d) | Both b and c |
| 56 | A lossless line having characteristic impedance Z_0 is terminated with a load impedance of jZ_0 . VSWR of the line will be : | | | |
| | a) | 1 | b) | 10 |
| | c) | Infinite | d) | None of the above |
| 57 | A signal $1 + \cos(2\pi ft) + \cos(6\pi ft)$ where $f=1\text{MHz}$ is sampled at 3MHz and Fourier Transform is carried out. How many lines will be seen in Fourier Transform? | | | |
| | a) | 5 | b) | 1 |
| | c) | 3 | d) | 2 |
| 58 | The array factor of an array antenna depends on | | | |
| | a) | Number of radiating elements | b) | Spacing between the elements |
| | c) | Phase of the applied signal | d) | All of the above |
| 59 | Which of the following parameter is improved by introducing pipelining in digital design? | | | |
| | a) | Area (Gate count) | b) | Maximum clock frequency |
| | c) | Power dissipation | d) | Noise |
| 60 | A transmission line having characteristic impedance ' Z_t ' of varying length in series with a load impedance ' Z_L ' appears in a Smith Chart on: | | | |
| | a) | Constant Resistance Circle | b) | Constant VSWR Circle |
| | c) | Constant Reactance Circle | d) | All of the above |
| 61 | Impedance characteristics on a Smith Chart repeat after a distance of: | | | |
| | a) | λ | b) | $\lambda/4$ |
| | c) | $\lambda/2$ | d) | None of the above |




INDIAN SPACE RESEARCH ORGANISATION

Page 11 of 18


| | | | | |
|----|---|------------------|----|--------------------|
| 62 | If τ is the time constant and ω is the applied frequency, a low pass RC filter acts as a pure integrator when: | | | |
| | a) | $\omega\tau=0$ | b) | $\omega\tau \gg 1$ |
| | c) | $\omega\tau = 1$ | d) | $\omega\tau \ll 1$ |
| 63 | 10 μ F capacitor is connected across secondary winding of a high frequency transformer having primary to secondary turns ratio 5:2. What is the value of capacitance seen across primary? | | | |
| | a) | 4 μ F | b) | 62.5 μ F |
| | c) | 25 μ F | d) | 1.6 μ F |
| 64 | What will be the output of the following circuit, if point-P is stuck at 1? | | | |
| | | | | |
| | a) | $A+B+C$ | b) | $A'B'C'$ |
| | c) | $(ABC)'$ | d) | 0 |
| 65 | For the current mirror circuit shown below, if the emitter area of Q2 is thrice of Q1, the current I is: | | | |
| | | | | |
| | a) | 0.328mA | b) | 2.955mA |
| | c) | 0.105mA | d) | 0.012mA |
| 66 | Output of an Op-amp is 1V peak, and slew rate is 5V/ μ s. The maximum frequency of input sinusoidal signal that can be reproduced is: | | | |
| | a) | 398Hz | b) | 796Hz |
| | c) | 796KHz | d) | 398KHz |

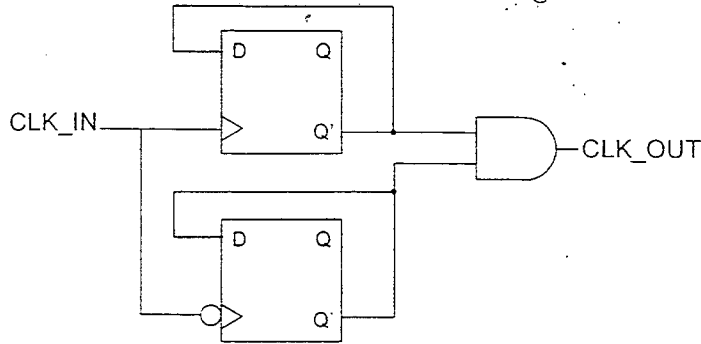67 What is the division factor of the following clock divider circuit?



- | | | | |
|----|-----|----|-----|
| a) | 2 | b) | 3 |
| c) | 1.5 | d) | 2.5 |

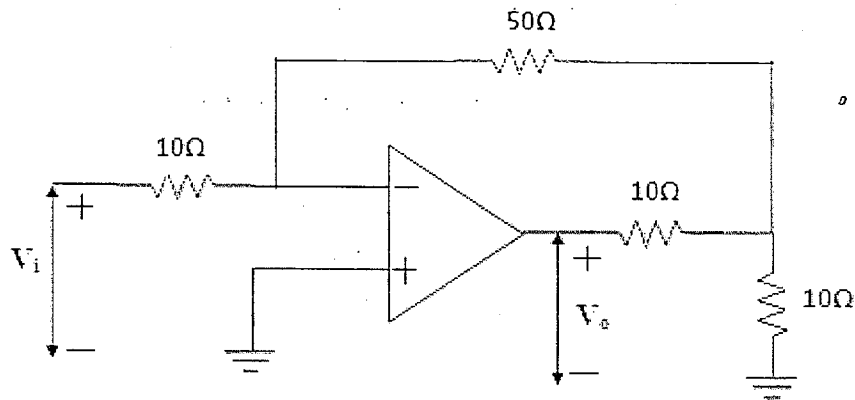68 For the circuit given below, the voltage V_o across the op-amp output is:




- | | | | |
|----|----------|----|---------|
| a) | $-9V_i$ | b) | $-3V_i$ |
| c) | $-11V_i$ | d) | $9V_i$ |

69 The rms value of current $i(t) = I_1 \sin \omega t + I_2 \sin 2\omega t$ is:

- | | | | |
|----|----------------------------|----|-----------------------------|
| a) | $(I_1^2 + I_2^2)^{1/2}$ | b) | $(I_1^2/2 + I_2^2/2)^{1/2}$ |
| c) | $(I_1^2/2 + 2I_2^2)^{1/2}$ | d) | $(I_1^2 + 4I_2^2)^{1/2}$ |



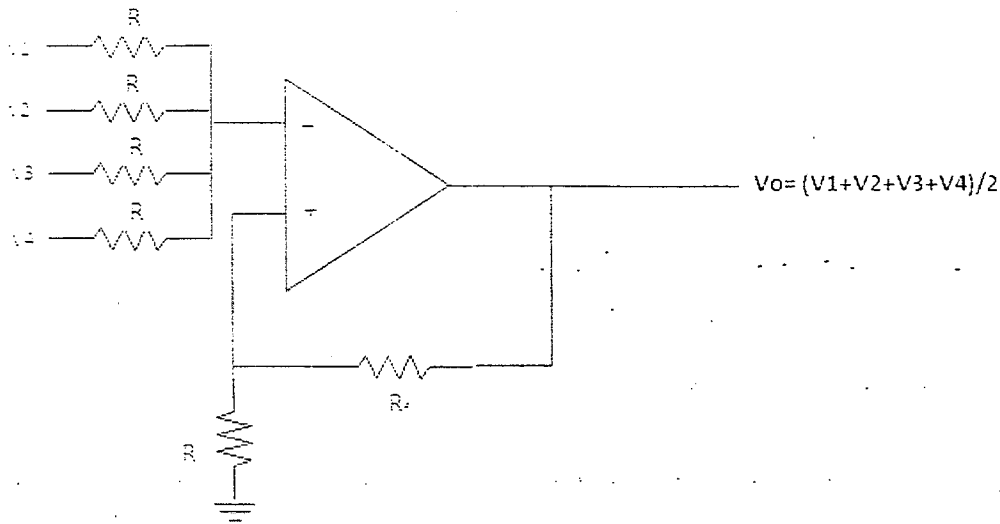70 Given the output for the following non-inverting summing amplifier, the relation between R_f and R in the circuit is:



- | | | | |
|----|----------|----|-----------|
| a) | $R_f=R$ | b) | $R_f=4R$ |
| c) | $R_f=2R$ | d) | $R_f=R/2$ |


71 A pulse signal having 100 kHz frequency and 70 nsec rise time is to be measured on an oscilloscope. The minimum required bandwidth of the oscilloscope is,

- | | | | |
|----|---------|----|----------|
| a) | 500 kHz | b) | 14.3 MHz |
| c) | 5 MHz | d) | 200 kHz |

72 Multiple collectors are used in Traveling Wave Tube (TWT) to :

- | | | | |
|----|--|----|------------------------------------|
| a) | To distribute the dissipated heat evenly | b) | To increase the overall efficiency |
| c) | To increase the gain of the TWT | d) | To shape the electron beam |

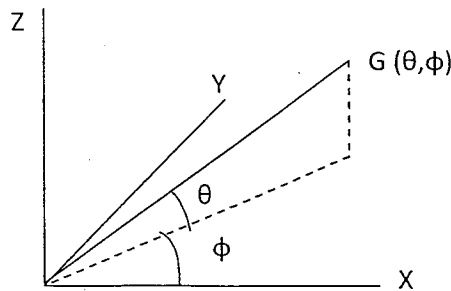73 A lossless antenna has directional gain $G(\theta, \phi)$, then $\int_{\phi=-\pi/2}^{\phi=\pi/2} \int_{\theta=-\pi/2}^{\theta=\pi/2} G(\theta, \phi) d\theta d\phi$ is :



ELECTRONICS - 2013









SET -A

| | | | | |
|---|---|---|----|--|
| | a) | 4π | b) | 2π |
| | c) | $\leq 4\pi$ | d) | $\leq 2\pi$ |
| 74 | $\sqrt[3]{\cos x - j\sin x}$ is equal to | | | |
| | a) | $(\cos x)^{1/3} - j(\sin x)^{1/3}$ | b) | $\sqrt[3]{\cos^2 x - j\sin^2 x}$ |
| | c) | $\cos \frac{x}{3} - j\sin \frac{x}{3}$ | d) | $\sin \frac{x}{3} - j\cos \frac{x}{3}$ |
| 75 | If $f(t)$ is 1 MHz sinusoid with 1 Vp-p and sampling frequency f_s is 25KHz, the output will be : | | | |
| <p>The diagram shows a signal $f(t)$ entering an 8-bit A/D converter. The output of the A/D converter is connected to an 8-bit D/A converter. The output of the D/A converter is labeled 'Output'. An arrow labeled f_s, Sampling Frequency, points to the A/D converter.</p> | | | | |
| | a) | 0V | b) | DC value anywhere between -1V and +1V |
| | c) | DC value anywhere between -0.5V and +0.5V | d) | 1Vp-p 1MHz sinusoid |







INDIAN SPACE RESEARCH ORGANISATION

Page 15 of 18

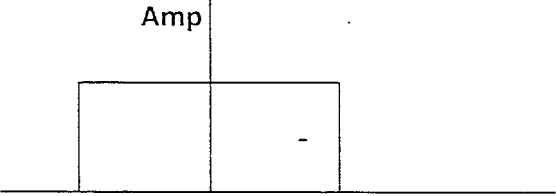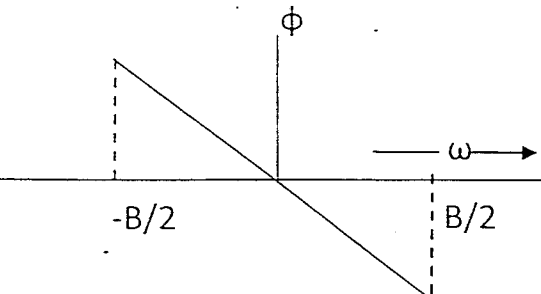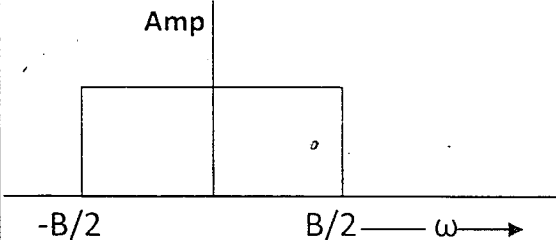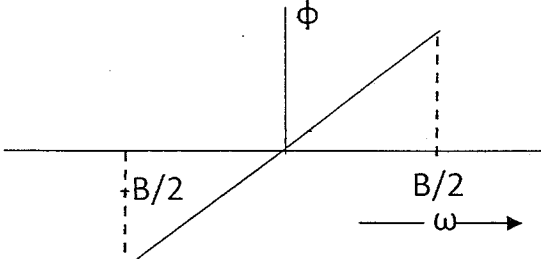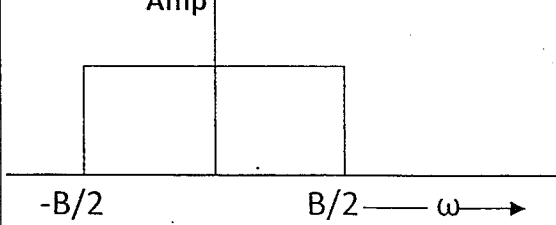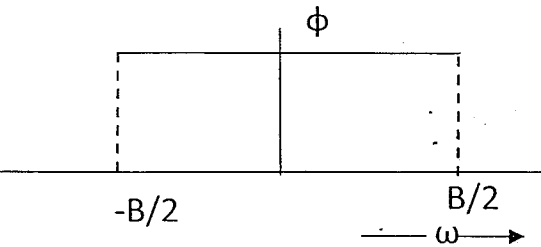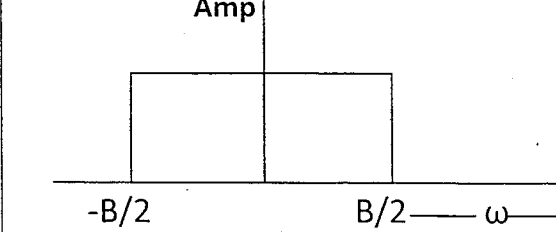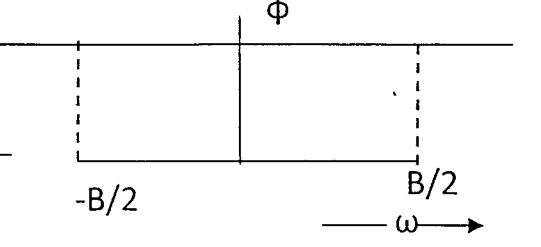
| | | |
|----|---|--|
| 76 | For a practical low pass filter , the ideal amplitude and phase response will be : | |
| a) |  |  |
| b) |  |  |
| c) |  |  |
| d) |  |  |

ELECTRONICS - 2013 SET -A
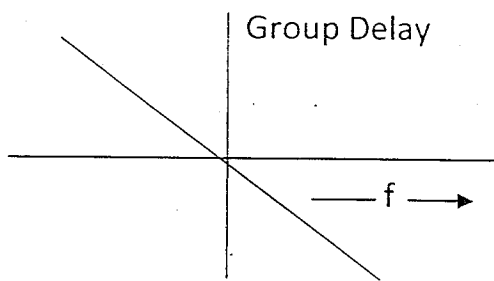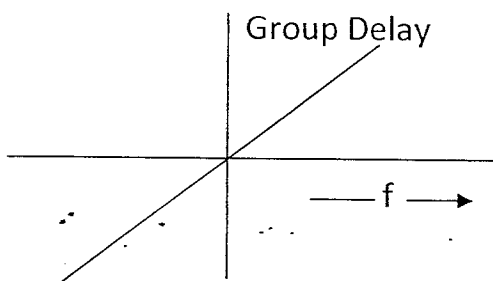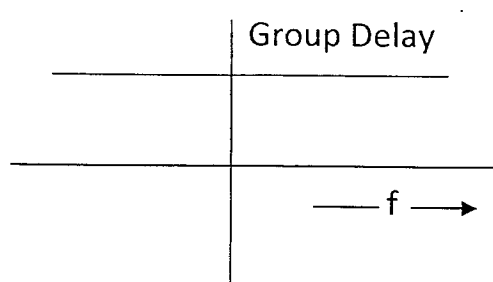
| | | | |
|----|--|--|--|
| 77 | A 10dB attenuator is put at the input of a low noise amplifier having 3dB noise figure. Now the noise figure of the cascaded amplifier will be | | |
| | a) 3dB | b) 12dB | |
| | c) 7dB | d) None of the above | |
| 78 | A 33.33% duty cycle rectangular wave is fed to the input of an Spectrum Analyzer. What will be observed? | | |
| | a) 2 nd , 5 th , 8 th harmonics missing | b) 3 rd , 6 th , 9 th harmonics missing | |
| | c) 1 st , 4 th , 7 th harmonics missing | d) All the harmonic present | |
| 79 | Phase function of a filter is $(f) = kf^2, k > 0$. The group delay of the filter has the shape | | |
| a) |  | | |
| b) |  | | |
| c) |  | | |
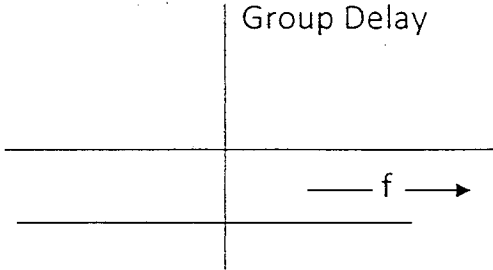
| | | |
|----|---|--|
| | d) |  |
| 80 | 1V p-p sinusoid is digitized by a 4 bit A-to-D converter with input dynamic range of 2V p-p. The signal to noise ratio of the digitized signal is : | |
| | a) | 384 |
| | b) | 96 |
| | c) | 48 |
| | d) | 24 |

End of questions

| | | |
|---|------------------------------------|---------------|
|  | INDIAN SPACE RESEARCH ORGANISATION | Page 18 of 18 |
|---|------------------------------------|---------------|