

Register Number

--	--	--	--	--	--	--

II Semester Diploma Examination, April/May-2015

ANALOG ELECTRONICS

Time : 3 Hours]

[Max. Marks : 100

- Note :** (i) Section – **I** is *compulsory*.
(ii) Answer any **two** full questions from of the remaining sections.

SECTION - I

1. (a) Fill in the blanks : **1 × 5 = 5**
- (i) A semiconductor has _____ temperature coefficient of resistance.
 - (ii) The element that has the biggest size in a transistor is _____.
 - (iii) A JFET is a _____ driven device.
 - (iv) An oscillator employs _____ feedback.
 - (v) An emitter follower has _____ input impedance.
- (b) Derive the relationship between alpha and beta in case of transistor. **5**

SECTION - II

2. (a) Explain the phenomenon of conduction in p-type and N-type semiconductor material. **8**
- (b) Explain the formation of PNP and NPN transistor. **4**
- (c) Mention the sketches of different types of transistor configuration. **3**
3. (a) Explain with sketch the construction and working operation of JFET. **8**
- (b) List the various types of electron emission and explain any one type of electronic emission. **7**
4. (a) Explain with neat sketch the working of LED. **6**
- (b) Explain with neat circuit diagram the zener diode as a voltage regulator. **4**
- (c) Explain with sketch the working of photo multiplier. **5**

[Turn over

SECTION - III

5. (a) Explain with neat circuit diagram the working operation of Bridge Rectifier. **8**
(b) Explain the working of Pi type filter. **7**
6. (a) Explain with neat circuit diagram the working operation of Class-B push pull amplifier. **8**
(b) Explain the faithful amplification and how it is achieved in transistor amplifier. **7**
7. (a) Explain with circuit diagram the working of Hartley oscillator. **7**
(b) List the advantages of oscillator. **4**
(c) List the advantages of negative feedback in transistor amplifier. **4**

SECTION - IV

8. (a) Explain with neat circuit diagram the VI characteristic of Zener diode. **8**
(b) State the difference between FET and Bipolar transistor. **7**
9. (a) List the advantages and disadvantages of integrated circuit. **6**
(b) Define the terms :
SSI, MSI, LSI, VLSI **4**
(c) With neat sketch explain the fabrication of transistor in IC technology. **5**
10. (a) Explain the working of Op-Amp as non inverting amplifier. **6**
(b) List the Ideal characteristic of an Op-Amp. **5**
(c) Explain the use of Op-Amp as running amplifier. **4**
-