

Register Number

--	--	--	--	--	--	--

II Semester Diploma Examination, April/May-2015

ELECTRICAL CIRCUITS

Time : 3 Hours]

[Max. Marks : 100


- Note :** (i) Section – I is compulsory.
 (ii) Answer any **two** full questions from the remaining Sections – II, III and IV.

SECTION - I

1. (a) Fill in the blanks : 5
- (i) Resistors, Inductors and capacitors are called _____ elements.
 - (ii) Relative permeability of air is equal to _____.
 - (iii) The average value of alternating voltage is _____.
 - (iv) The reciprocal of impedance is called _____.
 - (v) Power in 3- ϕ Y connected system is given by $P =$ _____.
- (b) Compare the magnetic circuit with the electric circuit. 5


SECTION - II

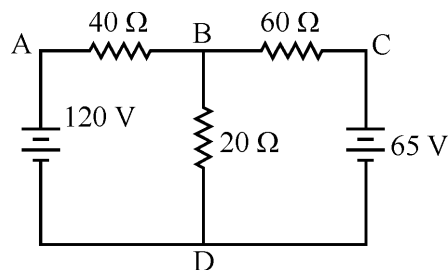2. (a) Define the following : 5
- (i) Unilateral circuit
 - (ii) Passive Network
 - (iii) Branch
- (b) State and explain KVL. 4
- (c) Find the magnitude and direction of current following through BD branch of the given Network using KVL : 6



[Turn over

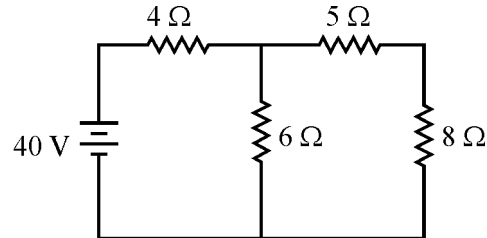3. (a) Explain about the ideal voltage source & practical voltage source. 4
 (b) State and explain Thevenin's Theorem. 5
 (c) Using Thevenin's Theorem. Find the current through $6\ \Omega$ Resistor in the given circuit below. 6



4. (a) State and explain the Maximum power transfer Theorem. 5
 (b) Explain the following terms :
 (i) Permeability
 (ii) Reluctance
 Mention the units. 4
 (c) An iron ring has mean circumferential length of 60 cm. with an air gap of 1 mm and a uniform winding of 300 turns with a current of 1A flows through the coil. Find the flux density. Take the relative permeability of iron is 300. 6

SECTION - III

5. (a) Define self and mutual inductance. 4
 (b) State and explain Lenz's Law. 5
 (c) Describe magnetic field around a current carrying conductor. 6
6. (a) Define the following terms and maintain their units of a sinusoidal wave : 4
 (i) Amplitude
 (ii) Frequency
 (b) Explain RMS value and average value of A.C. sine wave. 5
 (c) A voltage waveform given by the expression $v = 200 \sin (628 t + 60^\circ)$
 Determine :
 (i) Maximum value
 (ii) RMS value
 (iii) Frequency 6

7. (a) Convert the value of given vector from rectangular to polar and Polar to rectangular. 4
- (i) $200 + j 700$
- (ii) $8 \angle 90^\circ$
- (b) Two impedances $Z_1 = 20 + j 10$ and $Z_2 = 8 + j 20$ are connected in parallel. Find the magnitude of total impedance and power factor of the circuit. 5
- (c) Two Phasors are given $V_1 = 4 + j 3$ and $V_2 = 5 + j 6$. 6
- Find :
- (i) $V_1 \times V_2$
- (ii) $\frac{V_1}{V_2}$

SECTION - IV

8. (a) Define the following : 7
- (i) Impedance
- (ii) Inductive reactance
- (iii) Power factor
- (iv) Capacitive reactance
- (b) A series R-L-C circuit has $R = 10 \Omega$, $L = 5 \text{ mH}$ and $C = 100 \mu\text{F}$ is supplied with 200 V, 50 Hz. Find the current, power and power-factor of the circuit. 8
9. (a) Compare the Single Phase and Three Phase system. 4
- (b) Derive the relationship between Line Voltage and Phase Voltage in 3-phase star system. 5
- (c) Three impedances each of containing 20Ω resistance and 15Ω inductive reactance in series; connected in delta across 400 V, 3-phase supply. 6
- Calculate :
- (i) Line current
- (ii) Phase current
- (iii) Total power consumed

[Turn over

10. (a) State and explain Faraday's Laws of Electromagnetic Induction. **5**
- (b) Draw an A.C. sine wave and mark the following : **5**
- (i) Peak value
 - (ii) RMS value
 - (iii) Cycle
 - (iv) Instantaneous value
- (c) Define Absolute Permeability and relative Permeability and mention their units. **5**
-