

Code: A-27

Subject: DIGITAL HARDWARE DESIGN

Time: 3 Hours

Max. Marks: 100


NOTE: There are 11 Questions in all.

- Question 1 is compulsory and carries 16 marks. Answer to Q. 1. must be written in the space provided for it in the answer book supplied and nowhere else.
- Answer any THREE Questions each from Part I and Part II. Each of these questions carries 14 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or best alternative in the following: (2x8)

- a. In a strongly connected machine
- (A) every state has same output
 (B) all states are compatible
 (C) every state is reachable from all states
 (D) there exists a terminal state
- b. Which of the following functions is symmetric function
- (A) $x'y'z + xy'z' + x'yz'$. (B) $x'y'z + xy'z'$.
 (C) $x'y'z + xyz'$. (D) $x'y'z' + x'yz' + xy'z'$.
- c. In an 8-bit ring counter the preloaded pattern repeats after
- (A) 8 clock pulses. (B) 16 clock pulses.
 (C) 4 clock pulses. (D) 6 clock pulses.
- d. The frequency of the clock generated by the statement “clk \leftarrow not clk after 10 ns”; is
- (A) 50 MHz. (B) 5 MHz.
 (C) 500 MHz. (D) 33 MHz.

 - e. For the merger graph shown in the compatible state pairs are



- (A) (AB); (AC); (CD)
 (B) (ABC); (CD)
 (C) (AD); (AB); (AC)
 (D) (ABCDE)
- f. The ASM chart shown in Fig.2 represents


- (A) MOD-2 counter
 (B) MOD-3 counter
 (C) MOD-4 counter
 (D) MOD-5 counter



g. Time delay in an FPLA is

- (A) more as compared to PAL
- (B) less as compared to PAL
- (C) equal to PAL
- (D) zero

 h. $F = \bar{B}D + \bar{A}B\bar{C} + A\bar{C}D + \bar{A}BC$ represents the switch expression represents the complementary function of



one of the following

- (A) $\bar{E}\bar{D} + A(\bar{D} + B\bar{C})$
- (B) $\bar{A}B + \bar{B}D + \bar{C}\bar{D}$
- (C) $\bar{A}\bar{B} + B\bar{C} + \bar{C}\bar{D}$
- (D) $\bar{A}B + \bar{B}C + \bar{C}\bar{D}$

PART I

Answer any THREE Questions. Each question carries 14 marks.

Q.2 a. Determine

- (i) canonical sum-of-products form for $f(x, y, z) = x'y + z' + xyz$.
- (ii) canonical products-of-sums form for $f(x, y, z) = x'(y' + z)$. (4)

b. What do you understand by functionally complete operation? Prove that NAND and NOR operations are functionally complete. (4)

c. For the function $f(w, x, y, z) = \sum (0, 1, 2, 3, 4, 6, 7, 8, 9, 11, 15)$ find all prime implicants and indicate which are essential. Find a minimal expression for f. (6)

Q.3 a. Design a code converter which converts a BCD message into Excess-3 code. Realize this code converter using an appropriate ROM. (8)

b. Draw the output logic macro cell (OLMC) of a GAL and explain its function. (6)

Q.4 a. Design a mod-8 counter which counts in gray code. Realize it using D flip-flop. (6)


b. A synchronous sequential circuit has two JK flip-flops A and B with positive edge clock inputs, two input variables x and y and one output variable z. The flipflop input functions and circuit output function are given as $J_A = Bx + \bar{B}y$, $K_A = \bar{B}xy$, $J_B = \bar{A}x$, $K_B = A + x\bar{y}$, $z = Axy + B\bar{x}y$. For the synchronous sequential circuit described

- (i) draw logic diagram.
- (ii) derive next state equations for A and B.
- (iii) construct state table. (8)

Q.5 a. Write behavioural VHDL code for 4-bit comparator with 6 bit output Y[0:5] where bits 0 to 5 represent equality, in-equality, greater than, less than, greater than or equal and less than or equal outputs respectively. (7)

b. Design 4:16 decoder using 2:4 decoder with structural VHDL modelling. (7)

 Q.6 a. For the circuit shown in Fig.3 construct transition table and determine all critical and non critical races. Explore the possibility of cycles. (10)



b. Draw the portion of an ASM chart starting from an initial state. There are two control signals x and y. If $xy=10$, register R is incremented by one and control goes to a second state. If $xy = 01$, R is cleared to zero and control goes from initial state to a third state otherwise control stays in the initial state. (4)

PART II

Answer any THREE Questions. Each question carries 14 marks.

Q.7 a. Find the reduced state table for the machine given below: (9)

PS	NS, Z_1Z_2			
	00	01	11	10
A	A, 00	E, 01	-, -	A, 01
B	-, -	C, 10	B, 00	D, 11
C	A, 00	C, 10	-, -	-, -
D	A, 00	-, -	-, -	D, 11
E	-, -	E, 01	F, 00	-, -
F	-, -	G, 10	F, 00	G, 11
G	A, 00	-, -	-, -	G, 11

b. Define fundamental mode and pulse mode of operations for a sequential machine. (5)

Q.8 a. Give a simple state assignment by choosing self dependent subset and utilizing partition with substitution theory for the machine given below: (9)

PS	NS		Z
	x=0		x=1
A	D		C 1

B	A	D	0
C	B	E	0
D	E	B	0
E	F	C	0
F	C	D	0

- b. The sequential machine shown below has a closed partition $\pi = \{\overline{A, C, D, F} ; \overline{B, E, G}\}$. Can you find another closed partition so that a parallel decomposition of the said machine is possible? **(5)**

PS	NS	
	x=0	x=1
A	F, 1	C, 0
B	E, 0	B, 1
C	D, 0	C, 0
D	F, 1	C, 1
E	G, 0	B, 0
F	A, 1	F, 1
G	E, 1	G, 0

- Q.9** a. Design a two bit up down counter and show its implementation using an appropriate PAL. **(4)**

- b. A system, consisting of two registers R_1 and R_2 and a flip flop E, counts the number of 1's loaded into R_1 and sets R_2 to that number. Draw the ASM chart for the system and design the control circuit using multiplexers. **(10)**

- Q.10** a. A sequential network examines a group of 4 consecutive inputs and produces an output $z=1$ if input sequence 0101 or 1001 occurs. The network resets after every four inputs. Draw a Mealy state graph for the network and write state table and reduce it. **(8)**

- b. Write VHDL code for 3-bit odd parity generator using dataflow description. **(6)**

- Q.11** Write short notes on any **TWO** of the following:

- (i) Digital design using CAD tools.
- (ii) Vertical and horizontal microprogramming.
- (iii) FPGA.
- (iv) Equivalence between Mealy and Moore Machines.

(2 x 7 = 14)