

- g. A combinational logic circuit that is used when it is desired to send data from two or more source through a single transmission line known as
- (A) decoder (B) encoder
(C) multiplexer (D) demultiplexer
- h. The m-bit parallel adder consists of
- (A) (m+1) full adders (B) m/2 full adders
(C) (m-1) full adders (D) m full adders
- i. A demultiplexer is also known as
- (A) data selector (B) data distributor
(C) multiplexer (D) encoder
- j. 2 KB of memory means, its capacity is
- (A) 2000×8 bits (B) 2000×10 bits
(C) 2048×8 bits (D) 2024×8 bits

**Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.**

- Q.2** a. Write a note on CAD tools. (7)
- b. State De Morgan's law and prove it using truth table (3)
- c. Prove the Boolean identity $XY'Z + XYZ + X'Y'Z = XZ + Y'Z$ (3)
- d. Construct the truth table for Boolean expression given below. (3)
 $y = x_1 x_2 + x_2 x_3$
- Q.3** a. Realize the logic function $A' + B' + C$ using NAND gates only. (4)
- b. Simplify the expression $Y = ((AB)' + A' + AB)'$ (4)
- c. Simplify the Boolean expression using K maps. (4)
 $Y = \prod M (0,1,3,5,6,7,10,14,15)$
- d. Construct full adder with two half adders and OR gate. (4)
- Q.4** a. Draw the circuit of UP/DOWN counter. (4)
- b. Explain briefly different types of registers. (4)

c. Implement the following function with a 8x1 multiplexer. (4)
 $Y(A, B, C, D) = \sum(0, 1, 2, 5, 9, 11, 13, 15)$

d. Distinguish between combinational and sequential circuits. (4)

Q.5 a. Compare Moore and Mealy machines. (6)

b. Write a VHDL code for FSM that can detect 1011 sequence. (5)

c. write note on assert and report statement in VHDL. (5)

Q.6 a. Write a short note on FPGA. (4)

b. Differentiate between: (4)

(i) Next statement and exit statement

(ii) Wait statement and process statement

c. Write a VHDL code for T Flip Flop using behavioral approach. (4)

d. Write VHDL code for binary to gray code converter using data flow style of modeling. (4)

Q.7 a. Construct a Moore machine which is equivalent to the Mealy machine given in table. (6)

Mealy Machine

Present State	Next State			
	input a = 0		input a = 1	
	state	output	state	Output
→ q1	q3	0	q2	0
q2	q1	1	q4	0
q3	q2	1	q1	1
q4	q4	1	q3	0

b. Write VHDL code for BCD to seven segment decoder. (5)

c. Write a short note on functions and procedures in VHDL. (5)

Q.8 a. Write short notes on the following: (4×4=16)

(i) PAL

(ii) Structural Style of modeling

(iii) Race Around Condition

(iv) VHDL classes and objects

Q.9 a. Write a note on ASM charts and ASM blocks (8)

b. Define micro instruction format. (8)