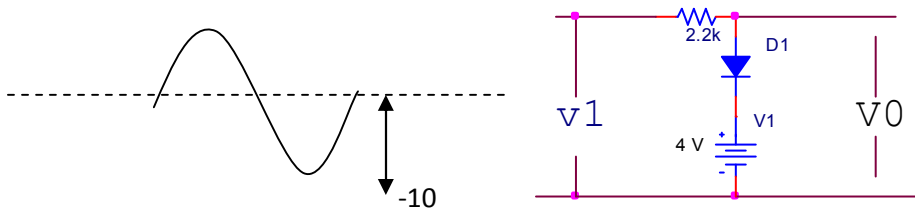


Question 1

- i) Do the following conversion
 - a. $A3E89_{16}$ to octal
 - b. $82B_8$ to hexadecimal
- ii) Subtract the following binary numbers:
 - a. $1100 - 1001$
 - b. $11010 - 10111$
- iii) Express -85 in 8 bit sign magnitude 1's and 2's complement form.
- iv) Add 56 and -27 using 2's complement form.
- v) The resistance of the semiconductor material decreases with an increase in temperature –Justify the following statement.
- vi) Distinguish between zener breakdown voltage and Avalanche breakdown . Which of the following can be used in the high voltage application?
- vii) Draw the output of the following circuit:



- viii) Bring out the difference between BJT and FET.
- ix) Draw the output of the following circuit.



x) If $\sqrt{41} = 5b$ find the value of b.

Question 2

Radiation falls on the semiconductor specimen that is uniformly illuminated, and a steady state is reached. At $t=0$, the light source is switched off. Sketch the minority carrier concentration as the function of time for $t \geq 0$. Define all the symbols in your equation describing the sketch.

Question 3


A crystal diode having an internal resistance $r_f = 20$ is used for half wave rectification. If the applied voltage is $v = 50 \sin 10t$ and the load resistance $R_L = 800$, determine the following:

- (i) I_m , I_{dc} and I_{rms} .
- (ii) AC power input and DC power output.
- (iii) DC output voltage
- (iv) Ripple factor.

Question 4


The BJT shown in the figure below has the following

All bypass and coupling capacitor assumed to have zero reactance at the signal frequency. Find the quiescent condition (V_{CEQ}, I_{CQ}) the small signal equivalent circuit the current, gain and input impedance seen by the current source I_C .

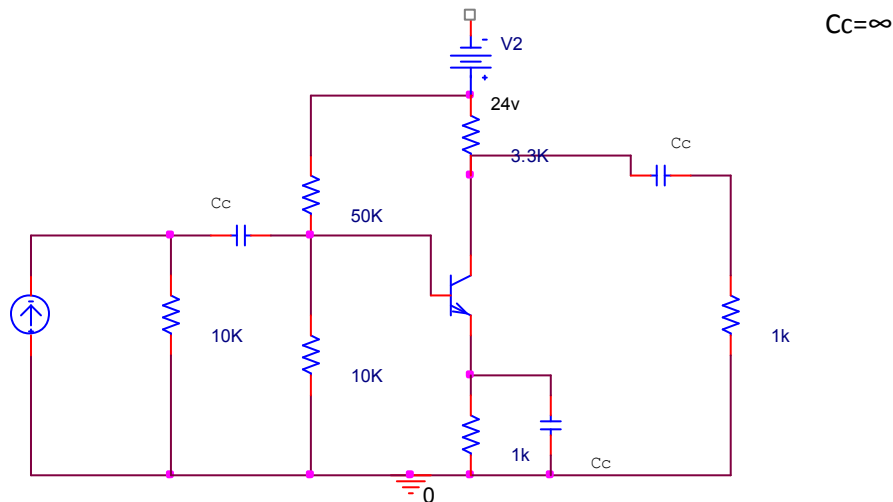

Question 5

Consider the opamp to be ideal . What would be the value of R for which the oscillation will be sustained? What is the frequency of oscillation?

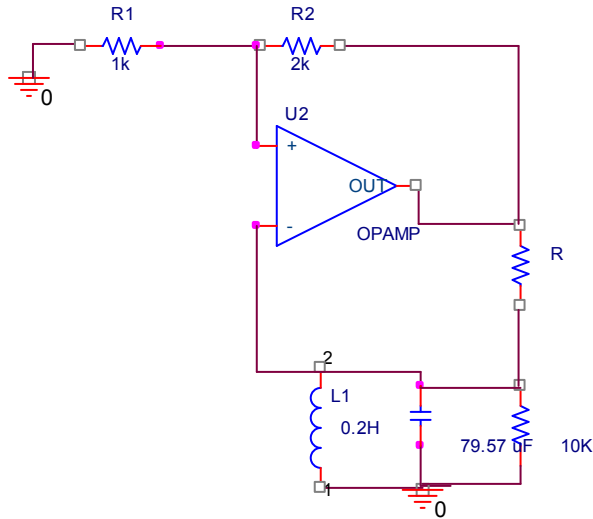

Question 6


- (i) Convert the following expression to canonical SOP form.(5)
 $(\bar{A}+C).(A.B+B.C+A.C)$
- (ii) Convert the following expression to canonical POS form.(5)
 $A+A.B+\bar{A}.C$

Question 7

For the emitter bias configuration of the following figure below with the following specification:

$$I_{CQ}=(1/2)C_{SAT} , I_{C sat} =8mA, V_e=18V$$

And $\beta = 110$, determine the value of R_c R_E and R_B .

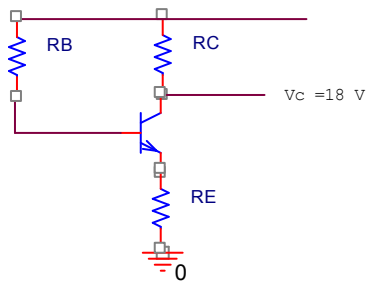

Question 8

- (i) Explain the need for the communication system . Hence describe the role of modulation and demodulation in it.(5)
- (ii) What is the input impedance of the ideal voltmeter and why? Explain CRO as a voltmeter?

Vgyan@com