

BT-5/D07

LINEAR IC APPLICATIONS

PAPER - ECE-307E

Time : 3 Hrs.

Maximum Marks : 100

Note : Attempt any five questions, selecting at least one from each unit.

UNIT-I


1. a. Define the common mode voltage, common mode voltage gain and common mode rejection ratio for Op-Amp. 5
- b. Draw and discuss the circuit of a Sample and Hold circuit. 5
- c. Explain the following parameters ; 10
 - (i) Slew rate
 - (ii) Input bias current
 - (iii) Output offset voltage
 - (iv) Supply voltage selection ratio
2. a. Sketch an Op-Amp non-inverting amplifier circuit. Also draw a basic Op-Amp circuit connected to function as a non-inverting amplifier. Explain the operation of the non-inverting amplifier and derive an equation for its voltage gain. 15
- b. What is Cascade amplifier ? List its characteristics. 5

UNIT-II

3. a. What is the difference between compensated and non-compensated Op-Amp. ? Draw the circuit of lag and lead compensation networks. Discuss this operation and show how they affect the frequency response of an Op-Amp. 15
- b. Draw the frequency response of operational amplifier. Why its gain roll-off often certain frequency ? 5
4. a. Describe the circuit of voltage of current converter, if the load is (i) floating, and (ii) grounded. Is there any information on the side of the load when grounded ? 10
- b. A non-inverting amplifier is to amplify 10mV signal to a level of 1 V using 741 Op-Amp. Design a suitable circuit and calculate its input and output impedances. 10

UNIT-III

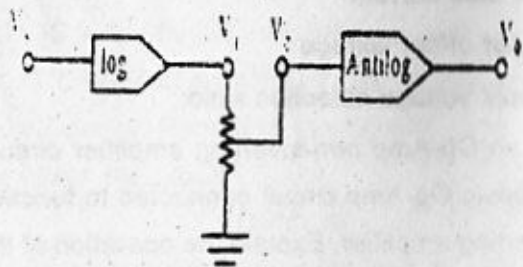5. a. Show that the following circuit can be used to raise the input V_S of an arbitrary power. Assume $V_1 = K_1 \ln K_2 V_S$, $V_0 = K_3 \ln^{-1} K_4 V_2$, $V_2 = \alpha V_1$. 15



- b. Name the circuit which can be used to detect the peak value of non-sinusoidal waveforms. Explain its operation

5

6. a. Sketch the circuit of a single stage band-pass filter. Discuss the low-pass and high-pass operation of the circuit. Show how band stop filter can be constructed by the use of band-pass filter and a summing circuit. 15
- b. Design a band-pass RC active filter with mid-band voltage gain of 30, centre frequency of 200 Hz, and $Q = 5$. Choose $C_1 = C_2 = 0.15 \mu\text{F}$. 5

UNIT- IV

7. a. Draw the block diagram of 555 timer IC. List its important features. 10
- b. What is the difference between digital and analog PLLs? 10
8. Write short notes on the following :
- 8038
 - PLL
 - Level translator circuit.
- 6, 7, 7