

Code: AE08  
Time: 3 Hours

Subject: CIRCUIT THEORY & DESIGN  
Max. Marks: 100

**DECEMBER 2010**

**NOTE:** There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after half an hour of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2x10)**

a. The voltage across the terminals AB in the Fig.1 is

- (A) 0.5 V
- (B) 3.5 V
- (C) 6 V
- (D) 6.5 V

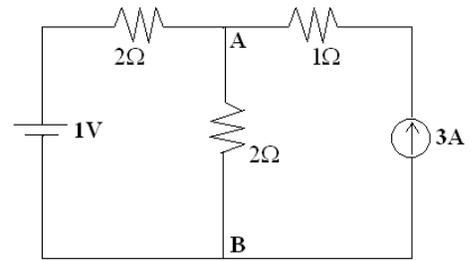


Fig.1

b. A tree of a graph must consist of

- |                          |                      |
|--------------------------|----------------------|
| (A) $b - n + 1$ branches | (B) $n - 1$ branches |
| (C) $b - n - 1$ branches | (D) $n$ branches     |

c. The transform network representation of the inductor with initial current is

- |  |  |
|--|--|
| (A) $V_L(s) = L_s I_L(s) + L I_L(0^-)$   | (B) $I_L(s) / L_s = V_L(s) + L I_L(0^-)$ |
| (C) $V_L(s) / L_s = I_L(s) + L I_L(0^-)$ | (D) $L_s I_L(s) = V_L(s) + L I_L(0^-)$   |

d. When the damping ratio  $\xi = 0$ , the poles of the system will be

- |                       |                         |
|-----------------------|-------------------------|
| (A) real and repeated | (B) real and unrepeated |
| (C) Complex conjugate | (D) imaginary           |

e. The rms value of a half wave rectified output is



- |                      |                       |
|----------------------|-----------------------|
| (A) $I_m / 2$        | (B) $I_m / \sqrt{2}$  |
| (C) $I_m / \sqrt{3}$ | (D) $I_m / 2\sqrt{3}$ |

f. The condition  $AD - BC = 1$  for a two port network implies that the network is a

- |                        |                                |
|------------------------|--------------------------------|
| (A) Reciprocal Network | (B) Lumped element Network     |
| (C) Lossless Network   | (D) Unilateral element Network |





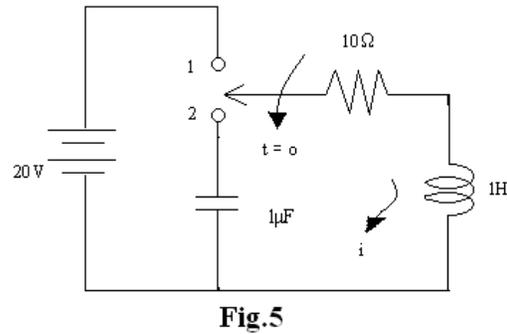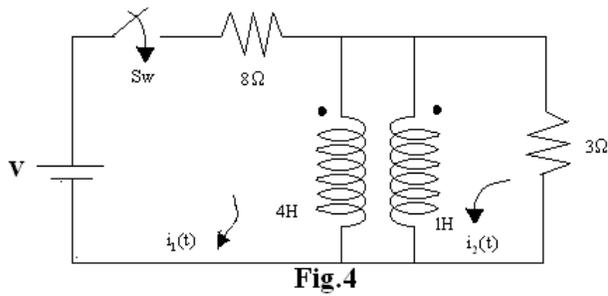- b. For the transformer circuit shown in Fig.4, the excitation  $v = 10 u(t)$ . Find  $i_1(t)$  and  $i_2(t)$  assuming  $i_1(0^-) = i_2(0^-) = 0$  (10)



- Q.4** a. In the circuit shown in Fig.5, switch k is changed from 20V to  $1\mu F$  at time  $t=0$ , steady state condition having been reached before switching, find the values of  $i$ ,  $\frac{di}{dt}$  at  $t=0+$ . (6)

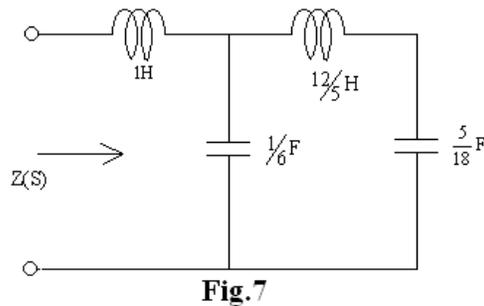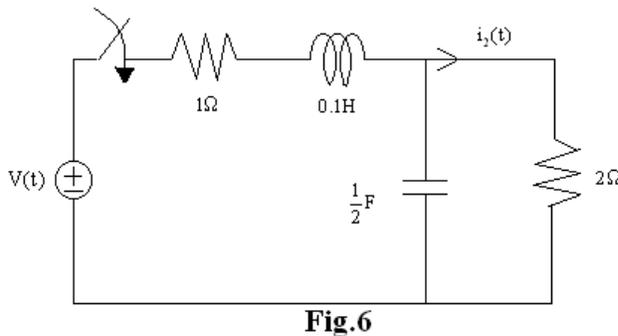
- b. In the network shown in Fig.6, the switch closes at  $t=0$ . If  $v(t) = 0.1 e^{-5t}$  and all the initial currents and voltages are zero. Find the current  $i_2(t)$  by Norton's theorem. (10)



- Q.5** a. For the network shown in Fig.7, find the transform impedance  $Z(s)$  in the factorised form. (10)

- b. Describe sine function using exponential excitation. (6)

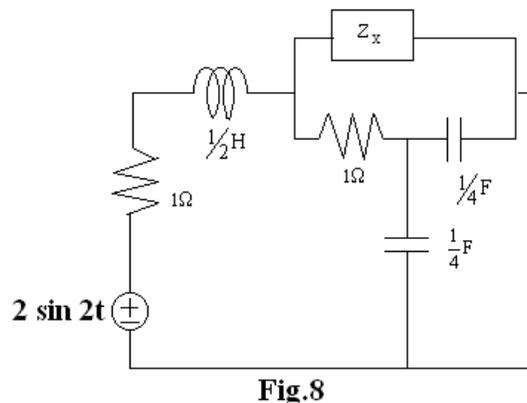- Q.6** a. For the network shown in Fig.8, determine the impedance  $Z_x$  such that maximum power is transferred from the source to load of impedance  $Z_x$  (6)




b. The system response of tuned circuit is given by  $H(s) = \frac{5}{s^2 + 2s + 5}$ .

Determine  $\omega_{\max}$ ,  $|H(j\omega_{\max})|$ , the half power point  $\omega_C$  and  $|H(j\omega_C)|$  (10)

**Q.7** a. Obtain Y parameters interms of Z- parameters (8)


b. Determine the h-parameters for the network shown in Fig.9. (8)

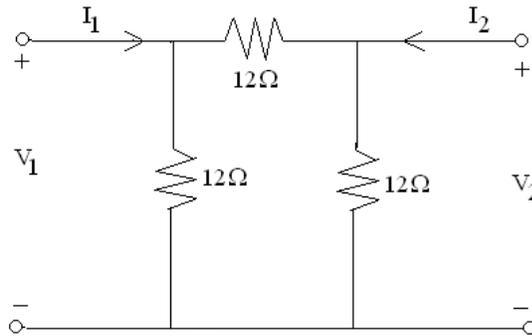

**Fig.9**

**Q.8** a. Determine whether the function  $F(s) = \frac{s^2 + 4}{s^3 + 3s^2 + 3s + 1}$  is a positive real function. (8)

b. For the network shown in Fig.10, find Y when  $\frac{V_2}{V_o} = \frac{1}{2 + Y} = \frac{s(s^2 + 3)}{2s^3 + s^2 + 6s + 1}$  synthesize Y as an LC – admittance. (8)

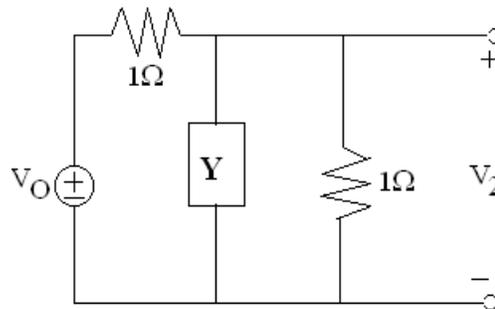

**Fig.10**

**Q.9** Determine the system fu: (16)

(i) Ripple of  $\frac{1}{2}$  db in band  $|\omega| \leq 1$

(ii) At  $\omega = 3$ , amplitude is down 30db