

(3 Hours)

[Total Marks : 100

- N.B.** (1) Question No. 1 is **compulsory**. Answer any **five** questions.
 (2) Assume **suitable** data if **required**.
 (3) Draw neat **diagrams** and **waveforms**

1. (a) List various electrical parameters of OP-AMP supplied in data sheet. 20
 (b) If GBP of OP-AMP is 2 MHz. What is its bandwidth when connected in voltage follower?
 (c) What is the difference between open loop and closed loop gain of OP-AMP?
 (d) Draw and explain circuit for missing pulse detector using timer 555.
2. (a) Draw circuit diagram for 3 OP-AMP Instrumentation amplifier. Explain how will you adjust gain by deriving an expression for output voltage. List all the features of Instrumentation amplifier. 10
 (b) Design Schmitt-Trigger circuit for : 10
 $UPT = 4V$, $LTP = 2V$, $V_{sat} = 12V$ using OP-AMP.
3. (a) Draw and explain circuit diagrams for following OP-AMP applications. Draw necessary waveforms (Any **two**) :— 10
 (i) Sample and Hold circuits
 (ii) Multiplier
 (iii) Voltage Limiter (positive and negative).
 (b) Draw circuit diagram for inverting and non-inverting comparator using OP-AMP. Draw necessary waveforms. 10
4. Draw circuit diagram for KRC LPF and derive its Transfer function. Find the expression for cut off frequency using equal component design. specify elements for 11th order LPF with $f_c = 1$ KHz and $Q = 5$. What is its d.c. gain? 20
5. (a) Draw and explain functional diagram for Astable Multivibrator using timer 555. 10
 (b) Draw circuit diagram for 1st order LPF using OP-AMP. Derive an expression for $\frac{v_o}{v_i}$. plot the frequency response for the same. 10
6. (a) Draw and explain functional block diagram for IC 8038. Write an equation for frequency of oscillation. 10
 (b) Explain the difference between active and passive filter. 10
7. Write short notes on any **four** of the following :— 20
 (a) PLL 4046
 (b) V-F Converter
 (c) OP-AMP noise
 (d) Internal Frequency Compensation
 (e) External Frequency Compensation
 (f) Generalized Impedance Converter.