

B. Tech Degree V Semester Examination, November 2009**EC/EI 505 MICRO ELECTRONICS AND INTEGRATED CIRCUITS**
(2006 Scheme)

Time : 3 Hours

Maximum Marks : 100

PART - A(Answer ALL questions)

(8 x 5 = 40)

- I. (a) Define the following terms :
- (i) Slew rate
- (ii) CMRR
- (b) Explain the working of integrator using op – amps.
- (c) Draw and explain the circuit of an astable multivibrator.
- (d) Draw and explain the circuit of a peak detector.
- (e) Draw the block diagram of PLL and explain each block.
- (f) Explain the working of Flash – type ADC.
- (g) What are the advantages of ICs over discrete components?
- (h) Differentiate between hybrid and monolithic integrated circuits.

PART – B

(4 x 15 = 60)

- II. (a) Draw the circuit of an op – amp inverting amplifier. Derive the expressions for voltage gain and input impedance. (10)
- (b) Explain virtual ground concept. (5)
- OR**
- III. Derive the expression for gain in an instrumentation amplifier. (15)
- IV. Explain the working of RC phase - shift oscillator using op – amp. Derive the expression for frequency of oscillation and gain. (15)
- OR**
- V. (a) Explain the working of Schmitt trigger and plot the transfer characteristics. (8)
- (b) Explain the working of all – pass filter. (7)
- VI. Explain the functional block diagram of 555 timer. How it can be used as monostable multivibrator. (15)
- OR**
- VII. (a) Explain the working of low voltage regulator using 723 IC. (10)
- (b) Explain the application of PLL as a frequency multiplier. (5)
- VIII. Explain bipolar IC fabrication steps with neat sketches. (15)
- OR**
- IX. Explain thick film technology. Explain how resistors and capacitors can be fabricated using thick film technology. (15)

