

Roll No.....

Total No. of Questions : 09]

[Total No. of Pages : 02

Paper ID [B0111]

(Please fill this Paper ID in OMR Sheet)

MCA (Sem. - 3rd)

COMPUTER SYSTEM ARCHITECTURE (MCA - 301)

Time : 03 Hours

Maximum Marks : 60

Instruction to Candidates:

- 1) Attempt any one question from Section - A, B, C & D.
- 2) Section - E is **Compulsory**.
- 3) Use of Non-Programmable **Scientific Calculator** is allowed.

Section - A

(1 × 10 = 10)

- Q1)** (a) Explain the JK master slave flip-flop.
(b) Simplify the expression $x = (A+B') (A'+B'+D')D$.
(c) Solve the expression $Z(A,B,C,D) = \sum(0,1,3,5,8,9,10,13,14,15)$ using K-map.
- Q2)** (a) Design a MOD 11 Counter using J-K Flip Flop and NAND Logic Gates.
(b) Design the 8-Bit full adder Circuit.

Section - B

(1 × 10 = 10)

- Q3)** Design the Arithmetic Circuit of a processor with truth table.
- Q4)** (a) - An 8-Bit register has one input x, the register operation is described symbolically as :

$$P : A_8 \leftarrow x, A_i \leftarrow A_i + 1 \quad i = 1, 2, 3, \dots, 7.$$

What is the function of the register? The cells are Numbered from right to Left.

- (b) Using the Quadruple 2 to 1 line Multiplexer and Four Inverters, Draw a Block diagram for implementing the statement.

$$T_1 : R_2 \leftarrow R_1$$

$$T_2 : R_2 \leftarrow R_2$$

$$T_3 : R_2 \leftarrow 0.$$

Section - C

(1 x 10 = 10)

- Q5)** (a) Write a micro program that compares two unsigned binary number stored in R_1 & R_2 . The register containing the greater number is then cleared. If the two numbers are equal, both numbers are cleared.
- (b) Explain the following :
- microoperation.
 - micro instructions.
 - microprogram.
- Q6)** A computer has 16 registers an ALU with 32 operations and a Shifter with eight operations all connected to common Bus system.
- Formulate a control word for a microoperation.
 - Specify the number of bits in each field of control word and give an encoding scheme.
 - Show the bits of the control word that specify the microoperation $R_4 \leftarrow R_5 + R_6$.

Section - D

(1 x 10 = 10)

- Q7)** (a) How many 128×8 RAM chips are needed to provide a memory capacity of 2048 bytes.
- (b) How many lines of address bus must be used to access 2048 bytes of memory? How many of these lines will be common to all chips.
- (c) How many lines must be decoded for chip select? Specify the size of decoders.
- Q8)** (a) Explain the Cache memory.
- (b) Explain Associative memory.

Section - E

- Q9)** a) Draw the logic circuit for $y = (a'+b'+c) (a'+b+c')$ using any of the universal Gate. (2)
- b) Suppose a ROM has 16 input address lines. How many memory location does it have, Range them. (2)
- c) Convert the 1234 BCD its Octal equivalent. (2)
- d) Name the various Addressing Modes for pointing a data in a memory location. (3)
- e) Explain the constituents of an Instruction Cycle. (3)
- f) What is a Virtual memory? (4)
- g) Differentiate between Microprogramming and Hardwired control unit. (4)

* * *