

AMIETE – ET (OLD SCHEME)

Code: AE12**Subject: INSTRUMENTATION AND MEASUREMENT****Time: 3 Hours****Max. Marks: 100****DECEMBER 2009****NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1 must be written in the space provided for it in the answer book supplied and nowhere else.
 - Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
 - Any required data not explicitly given, may be suitably assumed and stated.
-

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. Example of an active transducer is

- (A) strain gauge (B) LVDT
(C) piezoelectric transducer (D) resistance transducer

b. In an amplified dc meter, the role of the amplifier is to provide

- (A) high gain (B) large bandwidth
(C) high input impedance (D) low input impedance

c. The purpose of providing a varactor diode in a signal generator is to facilitate

- (A) amplitude modulation (B) tuning the main signal
(C) frequency multiplication (D) frequency modulation

d. For horizontal deflection system of a CRO, the waveform of voltage to be applied should be

- (A) rectangular (B) ramp
(C) impulse (D) sinusoidal

e. To extend the frequency range of a frequency counter one may use

- (A) a prescaler which is a digital counter
(B) an amplifier with suitable gain
(C) a comparator with zero crossing detection
(D) an amplifier with large bandwidth

f. Bolometer measures RF power using

- (A) magnetic field of RF
(B) heating effect of RF
(C) induced emf by RF field
(D) heterodyning with another RF source

- g. The receiver parameter 'image' refers to
- (A) reflection of RF from unmatched load
 (B) uncontrolled change in local oscillator frequency
 (C) spurious response to heterodyning process
 (D) shift of carrier frequency
- h. The IF amplifier used in spectrum analyzer is
- (A) a high gain large bandwidth amplifier
 (B) successive limiting type logarithmic amplifier
 (C) a narrow band tuned amplifier
 (D) a unity gain high input impedance amplifier
- i. An example of a magneto resistive material is
- (A) Quartz (B) Nichrome alloy
 (C) Bismuth (D) Mu-metal
- j. The input to an 8-bit A/D converter with 10 V reference is 3.797 volts. The digital output from the converter is
- (A) 1000 0011 (B) 0110 0001
 (C) 00110111 (D) 1001 1001

**Answer any FIVE Questions out of EIGHT Questions.
 Each question carries 16 marks.**

- Q.2** a. Distinguish between systematic and random errors in measurement systems. State briefly the scientific approaches to minimize these errors. (10)
- b. Define the term 'settling time' of an instrument and indicate the factors determining its value in a system. (6)
- Q.3** a. What are the advantages of using a chopper-stabilized amplifier in voltage measurements? Describe using a neat circuit diagram, the operation of a series-shunt chopper based on MOSFETs. (10)
- b. Find the values of C_X and R_X in the capacitance comparison bridge shown in Fig.1 below which is balanced with the following parameters. $R_1 = 12 \text{ K}\Omega$; $R_2 = 60 \text{ K}\Omega$; $R_3 = 120 \text{ K}\Omega$; $C_3 = 80 \text{ }\mu\text{F}$. (6)

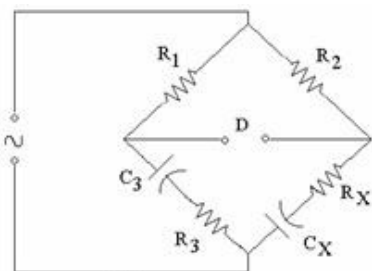


Fig.1

- Q.4** a. Why linearizing circuit is necessary? Explain using circuit diagram, the working of a linearizing circuit connected to a sweep generator. (8)

b. Draw block schematic of a frequency counter and delineate its operation. (8)

AB and BC are non reactive resistor of 100Ω each, DA is standard variable inductor L of resistance 32.7Ω and CD comprises a standard variable resistor R in series with a coil of unknown impedance. Balance

Q.5 a. Derive an expression for deflection sensitivity of a CRO with electrostatic deflection. (9)

b. What is the difference between 'dual-beam' and 'dual trace' oscilloscopes? Show a scheme to derive dual trace for a CRO and explain its operation. (7)

Q.6 a. Draw a neat figure to illustrate an experimental set-up to measure magnetic flux by measuring emf induced by the flux. (10)

b. Explain how RF power is measured by RF volt-meter. (6)

Q.7 a. Describe measurement set-up and procedure to measure sensitivity of a radio receiver by Quieting method. (7)

b. Explain Harmonic distortion. What are the causes by which harmonic distortion may result? Show a block schematic of heterodyne harmonic analyzer and explain its operation. (9)

Q.8 a. Taking a minimum of 4 bits inputs, show any one type of D/A converter and explain its operation. (8)

b. Draw a Hay's bridge circuit and obtain expressions for unknown inductance and resistance in one arm of the bridge. (8)

Q.9 a. Discuss applications of capacitive transducers for displacement measurement. Show a scheme of capacitive transducer in a bridge by which outputs proportional to linear displacements may be obtained. (10)

b. Find the bridge offset voltage in the strain gauge bridge shown in Fig.2 when a strain of $1450\mu\text{m}/\text{m}$ is applied on the SG, whose $GF = 2.03$ and nominal resistance is 350Ω . The bridge is balanced when the gauge is unstrained. (6)

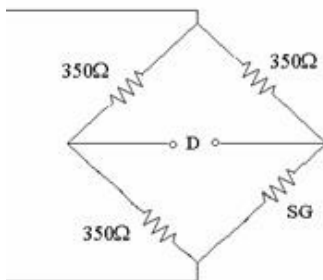


Fig.2