 



4
MODULE - V

- IX a) Explain the Basic principles of a Difference Amplifier & distinguish between
(i) Common signal Mode of operation &
(ii) Differential signal mode of operation.
Define CMRR. (10)
- b) Identify each Op-Amp stage & calculate the output voltages V_1, V_2 & V_3 . Calculate the currents I_1 & I_2 (10)




OR


- X a) Draw a schematic diagram of an Integrated circuit Op-Amp system & explain the function & important characteristics of each stage. (8)
- b) Compare the following characteristics of an Ideal Op-Amp with those of Real (practical Op-Amp by giving typical values.
(i) output offset voltage, (ii) Input Bias currents
(iii) Open loop voltage gain. (6)
- c) Determine the closed loop voltage gains & the input resistance of the Op-Amp circuits given (6)

 

 $A_{vf} =$
 $R_{in} =$
 $V_{01} =$
Calculate V_{01} & V_{02} .



$A_{vf} =$
 $R_{in} =$
 $V_{02} =$

 

Code No. BTS 005(C)

B.Tech. Degree III Semester Examination in Computer Science and Engineering, January 2001

CS 305 ELECTRONIC CIRCUITS

Time: 3 Hours

Max. Marks: 100


Instructions: 1) Answer 5 questions choosing one question from each Module.

2) Each question carries 20 marks

 3) Draw neat sketches, circuit diagrams, where they are required.

MODULE - I

- I a) Sketch the input and output characteristics of an NPN silicon Transistor & indicate the different regions of operation on the characteristics. Draw a suitable circuit which may be used to obtain the input & output characteristics of an NPN transistor in CE configuration. Write equations for the input current, output current and collector - emitter voltage, in the circuit that you have drawn. (10)
- b) Calculate the output collector current & I_{CEO} for an NPN transistor in CE configuration if $I_B = 50 \mu A$, $\beta = 80$, $I_{CBO} = 200nA$. (5)
- c) In the circuit shown calculate I_R, I_L & I_Z . Calculate the maximum power dissipation in the zener diode. (5)



OR


- II a) Explain the following with reference to JFET. (i) Pinch - off voltage, (ii) I_{DSS} , (iii) Gate - source cut off voltage (iv) Transconductance. (10)
- b) Draw an UJT circuit which can be used to obtain the Emitter characteristics. Draw a set of Emitter characteristics of an UJT & indicate all the salient features. (5)

(P.T.O)

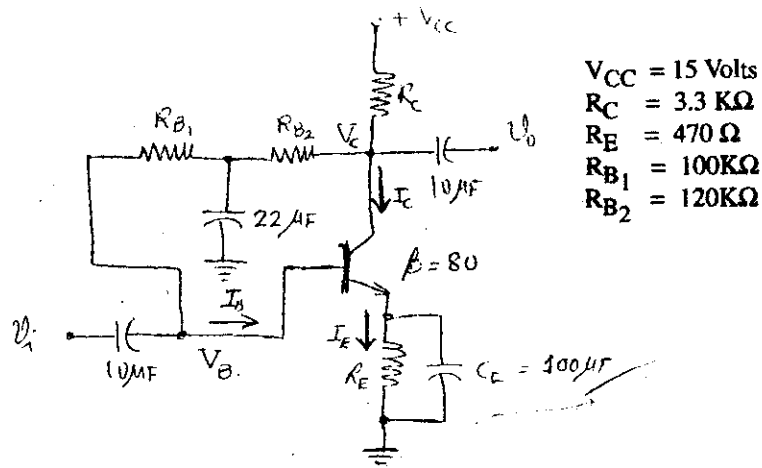- c) Write the "Shockley's equation" for the drain current of a JFET. Calculate I_D . If $I_{DSS} = 10\text{mA}$, & $V_p = 4\text{ Volts}$ at $V_{as} = -1\text{V}$ (5)

MODULE - II

- III a) Draw the following Transistor Biasing circuits & write equations to show the calculations of DC Quiescent state currents & voltages.
 (i) Fixed Bias Circuit
 (ii) Collector to Base Biasing Circuit. (10)
- b) Calculate $I_B, I_C, I_E, V_B, V_E, V_C$ & V_{CE} for the Transistor circuit shown. Assume the Transistor to be silicon. In what region does the Transistor operate? (10)



OR

- IV a) Sketch an RC coupled Amplifier circuit which is operated in the CE configuration & explain how this circuit operates as an amplifier. Draw the input base signal, collector current & collector voltage waveform. Indicate how you can draw the load line (DC) for the circuit you have drawn. (10)
- b) Draw a common Emitter Amplifier circuit using a voltage divider type of Bias - using the approximate h-parameter (10) equivalent circuit. Derive expressions for R_{in}, A_v, A_i & R_o

MODULE - III

- V a) What are the advantages of Negative Feed back ? With schematic diagrams illustrate the different types of Feed back mechanisms employed in amplifier circuits. (10)


Contd...3

- b) With suitable circuit diagrams, bring out the important differences between
 (i) Differentiating & Integrating circuits.
 (ii) Clipping & clamping circuits. (10)

OR

- VI a) With a neat sketch illustrate & explain the following pulse characteristics
 (i) Rise time (ii) Over shoot (iii) Ringing, (iv) Fall time & (v) under short. (10)
- b) Explain how an NPN silicon Transistor may be used as a switch.

 In the circuit shown, calculate the Maximum collector current, Maximum & Minimum collector voltages, when the input pulse is applied. Assume $V_{BE(sat)} = 0.7\text{ V}$ $V_{CE(sat)} = 0.1\text{V}$. Sketch the collector current & collector voltage wave forms assuming the Rise and fall times of i_c as equal to 25% of Input pulse width. (10)



MODULE - IV

- VII a) With suitable diagrams, explain the differences between Class-A, Class-B & Class-C types of Power Amplifiers. (10)
- b) Draw a complementary symmetry push pull circuit & explain its operation with relevant wave forms. (10)

OR

- VIII a) Explain with a neat schematic diagram how a sinusoidal oscillator can be built. Establish the Bark Hausen's criteria, for sustained oscillations, starting from Basic Fundamentals. (10)
- b) Calculate the Gain of the amplifier necessary so as to satisfy the Bark Hausen's criteria, if the Feed back used in the system is 5%. (5)
- c) Compare the LC oscillators with crystal oscillators. (5)

Contd...4