
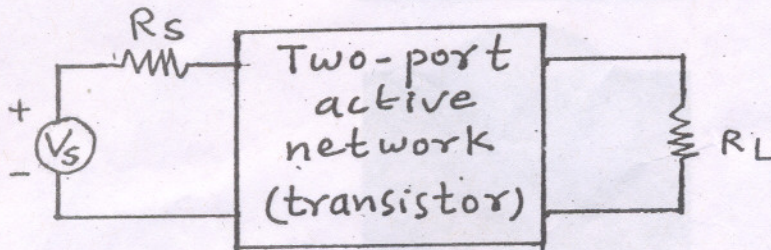


- N.B. (1) Question No. 1 is **compulsory**. Solve any **four** questions from the remaining.  
(2) Assume **suitable** data if **necessary**.

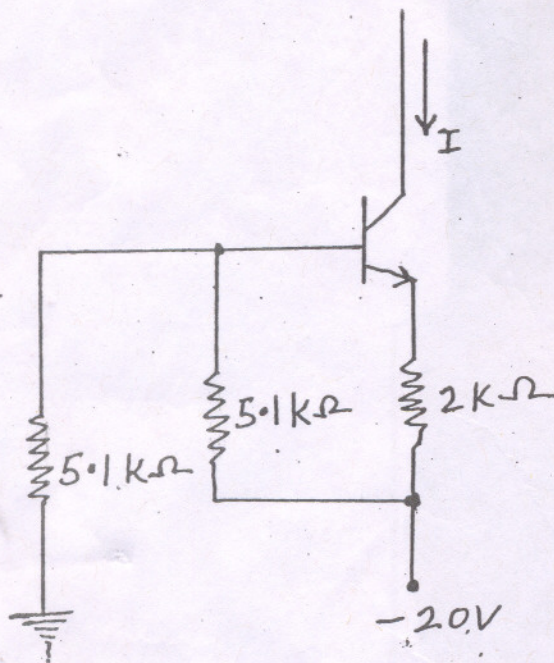1. The transistor is connected as a common emitter amplifier as shown in figure. Using small signal analysis find out,  $A_i$ ,  $R_i$ ,  $A_v$ ,  $A_{v_s}$ ,  $A_{i_s}$ ,  $Z_o$  and  $A_p$ .  
 $h_{ie} = 1100 \Omega$ ,  $h_{re} = 2.5 \times 10^{-4}$   
 $h_{fe} = 50$ ,  $h_{oe} = 25 \mu A/V$   
 $R_L = R_S = 1000 \Omega$ .



2. (a) Explain differential amplifier with constant current source using voltage divider network and current mirror. 10  
 (b) Determine the value of constant current and output resistance for the circuit of figure. 10



$$h_{fe} = 100$$

$$\frac{1}{h_{oe}} = 100 K\Omega$$

$$h_{ie} = 500 \Omega$$

3. (a) What is a function of a regulator? What is the difference between load regulation and line regulation? 8  
 (b) Using LM 723, design a continuously adjustable 2 V to 5 V supply with current limit of 1.0 A. 12
4. (a) Explain voltage controlled oscillator. How does it differ from a fixed frequency oscillator? Explain any one application of VCO. 10  
 (b) Explain the operation of the Wien bridge oscillator. Explain two ways to make the output frequency user adjustable. 10
5. (a) Determine the component values for a 2 KHz square wave generator with an 80% duty cycle using IC 555. 10  
 (b) Detail the differences between Flash Conversion and Successive Approximation Technique. What would each type be used? What are their limitations? 10



6. (a) Explain second order Butterworth active filter using OP-AMP. Give its frequency response curve. Give practical application of this filter. 10
- (b) Draw the circuit diagram of practical differentiator using OP-AMP. Give the disadvantages of basic differentiator. 10
7. Write short notes on any **two** :— 20
- (a) PWM IC voltage regulator
  - (b) Instrumentation amplifier using OP-AMP
  - (c) FET differential amplifier
  - (d) OP-AMP as Schmitt trigger and comparator.
-