

DISTANCE EDUCATION  
B.C.A. DEGREE EXAMINATION, DECEMBER 2010.  
ELECTRONIC DEVICES AND DIGITAL CIRCUITS  
(2003 onwards)

Time : Three hours

Maximum : 100 marks

Answer any FIVE questions.

1. (a) What is Excess-3 code? Why it is important? (5)
- (b) Write short notes on ASCII code. (5)
- (c) Convert the following :
  - (i)  $(5A8)_{16} = ?_2$
  - (ii)  $(555)_{10} = ?_8$
  - (iii)  $(741)_8 = ?_2$
  - (iv)  $(7400)_8 = ?_{10}$ . (10)
2. (a) "NOR gate is a universal building block" - Justify. (10)
- (b) What are the basic operations available in digital system? Explain with gate symbol. (10)
3. (a) Explain the function of Full Adder circuit. (10)
- (b) State and prove Demorgan's law with truth tables. (10)
4. (a) Simplify the function :
 
$$F(x, y, z) = \sum (0, 1, 3, 6, 7).$$
 (10)
  - (b) Using Demorgan's theorem, show that :
    - (i)  $(A + B)'(A' + B') = 0$
    - (ii)  $A + A'B + A'B' = 1$ . (10)

5. (a) Define Flip-flop. With neat diagram and truth-table explain the R-S flip-flop. (10)
- (b) Write short notes on Right shift and left shift operations. (10)
6. (a) Design a 2-bit shift register using JK flip flop. (10)
- (b) What are the various types of counters? Explain. (10)
7. (a) Explain the formation of the depletion region across an unbiased P-N junction. (10)
- (b) What are the different configurations of BJT? Explain. (10)
8. (a) Explain the construction of N-channel JFET. (10)
- (b) Explain the four distinct regions of the output characteristics of a JFET. (10)
-