

B.E. Sem 8 (REV.)

Power Electronics

02/12/08

WS Oct 08 193

Extra

Con. 5252-08.

(REVISED COURSE)

RC-7640

(3 Hours)

[Total Marks : 100

- N.B. :** (1) Question No. 1 is **compulsory**.  
(2) Attempt any **four** questions from remaining.  
(3) Assume **suitable** data if **necessary**.

1. (a) Is it possible to obtain Inversion mode operation in case of semiconverter feeding active load. Justify the answer. **20**  
(b) Compare IGST and SCR.  
(c) A thyristor is triggered by a pulse train of 5KHz. Duty Ratio of pulse train in is 0.5. If allowable average Gate Power is 100 watts. Calculate the true maximum allowable gate drive power.  
(d) Explain  $\frac{dv}{dt}$  and  $\frac{di}{dt}$  rating along with proper protection circuit for SCR.
2. (a) Explain pulse triggering method using UJT synchronized circuit for full wave (midpoint) configuration with neat diagram. **10**  
(b) In case of F.C.B.R. (single phase) feeding an active load, assuming constant output current. Draw the following waveforms : **10**  
(i) output voltage (ii) output current  
(iii) supply current (iv) voltage across any SCR.
3. (a) A 3 phase full wave converter bridge is connected to supply voltage of 230 V per phase and frequency of 50 Hz. The source inductance per phase i.e.  $L_s$  is 4 mH. The load current is 20 Amp. If the load consists of d.c. voltage source of 400 volt with internal resistance of  $1\Omega$ . Calculate : (i) firing angle delay (ii) overlap angle. **10**  
(b) Explain the operation of A.C. phase control circuit using Triac-Diac for 1amp. Dimmer applications. Draw the waveform across load. **10**
4. (a) Why commutation failure may occur in case of Jones chopper ? How it can be avoided ? **10**  
(b) In a basic step down d.c. chopper circuit Input voltage is 230 V,  $R = 10\Omega$ , drop across chopper is 2 volt. Duty cycle is 0.4. Determine : (i) Av. output voltage (ii) rms o/p voltage (iii) chopper efficiency. **10**

5. (a) Explain the operation of complementary commutation circuit. Draw the waveform across any one SCR and capacitor. 10
- (b) Explain the operation of basic series inverter and obtain an expression for turn off time available in terms of  $W_o$  and  $W_r$ . 10
6. (a) Explain microcontroller based closed loop speed control method of D.C. Motor. 10
- (b) Explain v/f control method for speed control of induction motor. 10
7. Write short notes on (any **three**) :- 20
- (a) Triggering circuit using IC TCA 785
  - (b) Performance parameters of uncontrolled rectifier
  - (c) Isolation technique
  - (d) IR compensation techniques.
-