

II B.Tech I Semester Regular Examinations, November 2007
ELECTRONIC CIRCUIT ANALYSIS
 (Common to Electronics & Communication Engineering and Electronics & Telematics)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Draw the circuit diagram of CB- amplifier and its h-parameter equivalent circuit. List out the characteristics of a CB amplifier.
 (b) In a single stage CB amplifier circuit, $R_E = 20K$, $R_C = 10K$, $V_{EE} = -20V$, $V_{CC} = 20V$, $R_L = 10K$ and $R_S = 0.5K$. Find A_I , R_i , R_o , A_V . (8+8)
2. (a) How multistage amplifiers are classified depending upon the type of coupling.
 (b) Write a note on distortions in amplifiers.
 (c) In an R-C coupled amplifier, $A_{VM} = 60$, $f_L = 50Hz$ and $f_H = 100KHz$. Find the values of frequencies at which the gain reduces to 50 on either side of mid band region. [4+6+6]
3. (a) What are the typical values of various components in Hybrid - π model? Show that at low frequencies the Hybrid - π model with $r_{b'e}$ and r_{ce} taken as infinite reduces to the approximate CE h- parameter model.
 (b) The following low- frequency parameters are known for a given transistor at $I_C = 10mA$, $V_{CE} = 10V$, and at room temperature,
 $h_{ie} = 500 \Omega$
 $h_{oe} = 4 \times 10^{-5} A/V$
 $h_{fe} = 100$
 $h_{re} = 10^{-4}$.
 At the same operating point, $f_T = 50MHz$ and $C_c = 3PF$, compute the values of all the Hybrid - π parameters [8+8]
4. (a) Define thermal resistance of a power BJT.
 (b) A transistor with a maximum junction temperature specification of $150^\circ C$ dissipates a maximum power of 40 watts at a case temperature of $25^\circ C$ and 2 watts at an ambient temperature of $25^\circ C$. Find
 - i. The thermal resistance between the junction and the case.
 - ii. The thermal resistance between the junction and ambient.
 - iii. Maximum power dissipation capability for safe operation in free space at a temperature of $50^\circ C$. [4+4x3]
5. (a) What is meant by the term Tuned amplifier and briefly explain the various methods of classification of tuned amplifiers?

- (b) A constant generator drives a parallel tuned circuit consisting of a lossless capacitor 'C' and a coil 'L' (having small resistance 'R'). Derive the expression for the frequency of resonance? [8+8]
6. (a) Explain the principle of a wideband amplifier?
- (b) Derive the expression for Optimum value of collector circuit resistor (R_C , opt) of one stage of a CE cascade amplifier. Draw the graph showing the variation of Bandwidth, Gain and Gain bandwidth product as a function of R_C and write the comments from the graph to improve the bandwidth. [4+12]
7. (a) With the help of a neat circuit diagram, explain the operation of BJT shunt voltage regulator.
- (b) What is a voltage reference? Why is it needed?
- (c) What is the function of a series pass transistor? [8+4+4]
8. (a) Explain how three terminal IC 7805 is used as a current source with a neat circuit diagram. [8]
- (b) What is a Voltage multiplier? Draw and explain any one circuit of it and give its applications. [8]
