

Third Semester B.E. Degree Examination, June / July 08 Electronic Instrumentation

Time: 3 hrs.

Max. Marks: 100

Note: 1. Answer any FIVE full questions, selecting atleast TWO questions from each part:

2. Assume any missing data.

- 1 a. Explain the following with example:
 - i) Gross Errors ii) Systematic Errors iii) Random Errors iv) Absolute Errors and v) Relative Errors. (10 Marks)
 - b. Find the voltage reading and % Error of each reading obtained with a voltmeter on i) 5 V range ii) 10 V range and iii) 30 V range, if the instrument has a 20 k Ω /V sensitivity and is connected across R_b. Comment upon the results. (10 Marks)

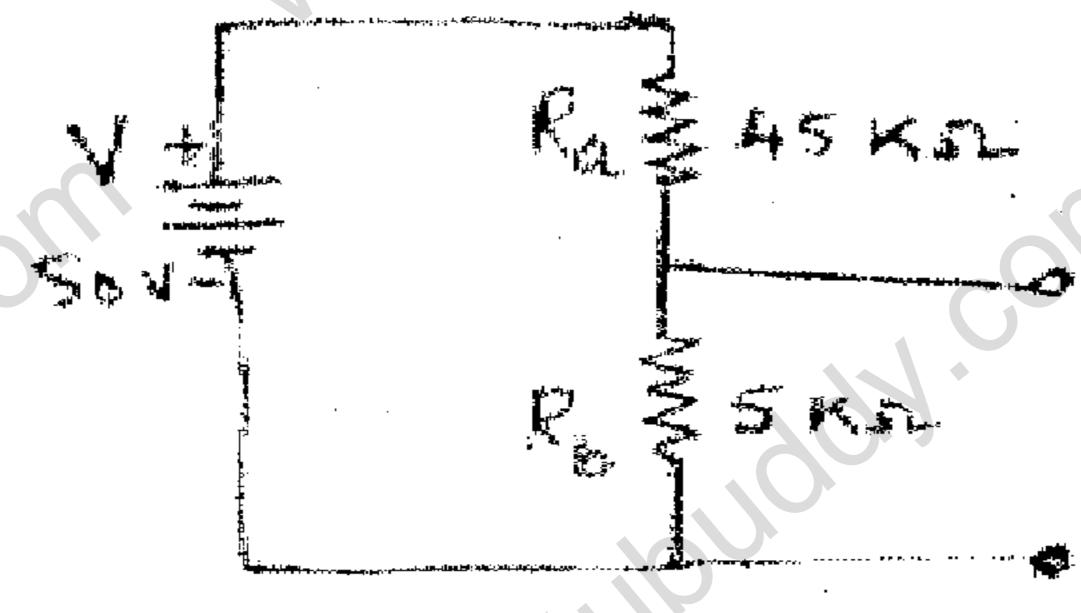


Fig.Q1(b)

- 2 a. With block diagram explain the principle and operation of successive approximation type DVM. Show transition diagram for 3 bit. (10 Marks)
 - b. With schematic explain the principle and operation of digital frequency meter. (10 Marks)
- a. Write typical CRT connection details and explain different control knobs on the front panel of the CRO. (10 Marks)
 - b. What is the difference between Dual beam and Dual trace CRO? (05 Marks)
 - c. An electrically deflected CRT has a final anode voltage of 2000 V and parallel deflecting plates 1.5 cm long and 5 mm apart. If the screen is 50 cm from the center of deflecting plates, find:

 i) Beam speed,

 ii) The deflection sensitivity of the tube and

 iii) The deflection factor of the tube.
- a. Explain the principle and operation of sampling oscilloscope. What are its advantages and disadvantages? (10 Marks)
 - b. With block diagrams explain the principle and operation of digital storage oscilloscope. Also explain how to overcome the limitations of this oscilloscope using high performance converter. (10 Marks)

PART B

- 5 a. With block diagram explain conventional standard signal generator. (10 Marks)
 - b. Explain with a block diagram AF Sine-Square wave audio oscillator with different knobs on the front panel. (10 Marks)
- 6 a. What are the limitations of Wheatstone's Bridge? Derive the balance equation of Kelvin's Double Bridge for unknown low resistance. (10 Marks)
 - b. Four arms of an AC bridge are as follows: AB = a pure capacitance of 0.2 μ F, $BC = 500 \Omega$ pure resistance, CD = unknown series circuit impedance, $DA = 0.1 \mu$ F capacitance in parallel with 300 Ω resistance. Arm BD is connected with a detector and 5 V, 1000 Hz supply is connected across AC. Find unknown components value which are in series in branch CD at bridge balance condition. Write circuit diagram. (10 Marks)
- 7 a. What are the factors to be considered for the selection of better transducer? Explain.
 (10 Marks)
 - b. Explain the construction, principle and operation of LVDT. Show characteristic curves. How is the direction of motion determined? (10 Marks)
- 8 a. What are the different types of photoelectric transducers? Explain any two. (10 Marks)
 - b. Explain the principle of LED and RTD. Comment on their characteristics. (10 Marks)